

## Certificate+ Diploma+ Advanced Diploma in Mechanical Engineering

### COURSE OBJECTIVES

<http://www.highlightcomputer.com/objectives.htm#a>

<http://www.highlightcomputer.com/objectives.htm#b>

### CURRICULUM & SYLLABUS

<http://www.highlightcomputer.com/Diploma%20&%20Advanced%20Diploma%20in%20Mechanical%20Engineering%20Course%20Detailed%20Contents.htm>

Mechanical Engineering Course Outline

### DETAILED CONTENTS

<http://www.highlightcomputer.com/Diploma%20&%20Advanced%20Diploma%20in%20Mechanical%20Engineering%20Course%20Detailed%20Contents.htm>

### ASSESSMENT POLICY

<http://www.highlightcomputer.com/assessmentpolicy.htm#a>

<http://www.highlightcomputer.com/assessmentpolicy.htm#b>

### **VIDEO LINKS**

<http://www.filefactory.com/file/3gv3i8yr2bhb/Instruction.mp3>

<http://www.filefactory.com/file/1b6itgv5drm7/Instruction.docx>

<http://www.filefactory.com/file/4flhf2uxiisf/Instruction.pdf>

### **Diploma + Advanced Diploma in Mechanical Engineering Videos**

<http://www.filefactory.com/file/17fxmu6rte7p/Part%202-Mechanical%20Video.mp4>

### Year (1)

### Certificate in Mechanical Engineering ( Each 1.5 Credits) ( 15 Pt )

| Unit Number               | Unit Name                                       | Credit Points |
|---------------------------|---|---------------|
| <a href="#">Maths 101</a> | <a href="#">Engineering Mathematics (EE201)</a> | 1.5           |

|                        |   |     |
|------------------------|---|-----|
| <a href="#">ME 101</a> | <a href="#">Applied Mathematics</a>             | 1.5 |
| <a href="#">ME 102</a> | <a href="#">Engineering Thermodynamics</a>      | 1.5 |
| <a href="#">ME 103</a> | <a href="#">Engineering Mechanics</a>           | 1.5 |
| <a href="#">ME 104</a> | <a href="#">Machine Principle</a>               | 1.5 |
| <a href="#">ME 105</a> | <a href="#">Electrical Principle</a>            | 1.5 |
| <a href="#">ME 106</a> | <a href="#">Electrical Circuits</a>             | 1.5 |
| <a href="#">ME 107</a> | <a href="#">Heat Transfer</a>                   | 1.5 |
| <a href="#">ME 108</a> | <a href="#">Principle of Engines</a>            | 1.5 |
| <a href="#">ME201</a>  | <a href="#">Introduction to Fluid Mechanics</a> | 1.5 |
|                        | Total   | 15  |

**Diploma in Mechanical Engineering ( Each 1.5 Credits) ( 15 Pt )**

[ME 202 Introduction to Aero Dynamics](#)

[ME 203 Control Engineering](#)

[ME 204 Engineering Fluid Mechanics](#)

[ME 205 Manufacturing Processes-and-Materials](#)

[ME 206 Introduction to Turbo Machinery](#)

[ME 207 Chemical Thermodynamics](#)

[ME 208 Hydrocarbons](#)

[ME 209 Introduction-to-polymer-science-and-technology](#)

[ME 234 Wind Turbines](#)

[Mgt 501 Basic Management](#)

**Year (2)**

**Advanced Diploma in Mechanical Engineering ( Each 1.5 Credits) ( 30 Pt)**

**Mathematics**

[Maths 403 Engineering-Mathematics \(EE302\)](#)

[Maths 301 Introductory Finite Difference Methods-for-pdes](#)

[Maths 302 Elementary-Linear-Algebra \(EE302\)](#)

[Maths 303 Introductory Finite Volume Methods-for-pdes](#)

[Maths 501 Linear Algebra-c-1 \(EE302\)](#)

### **Mechanical Engineering**

[ME 301 Fluid Dynamics](#)

[ME 302 Automation-and-Robotics](#)

[ME 303 Computer Aided Design and Manufacturing](#)

[ME 304 Introduction to Nonlinearity-in-control-systems](#)

[ME 305 Corrosion Prevention](#)

[ME 306 Theory-of-waves-in-materials](#)

[ME 334 Airconditioning and Refrigeration](#)

[ME 434 Mechtronics-Robotics](#)

[ME 534 Numerical Control](#)

[ME 634 Pneumatics](#)

[EE 617 Building Electrical and Mechanical System Part 1 \(EE309\)](#)

[EE 624 Process Control](#)

[Mgt 503 Production & Operation Management](#)

[Mgt 505 Quality Management and Manufacturing Engineering](#)

### **Bachelor of Engineering (Mechanical)**

### **Year (3)**

### **GENERAL APPLIED ENGINEERING (MECHANICAL) DEGREE**

|   |
|---|
| <b>Subjects</b>                                 |
| <b>BAE 401 Advanced Engineering Mathematics</b> |
| <b>BAE 402 Calculus</b>                         |

|   |
|---|
| <b>BAE 403 Engineering Mechanics</b>                              |
| <b>BAE 404 Engineering Materials &amp; Thermodynamics</b>         |
| <b>BAE 507 Electro-mechanical Energy Conversion</b>               |
| <b>BAE 508 Industrial Engineering &amp; Industrial Management</b> |
| <b>BAE511 Air-conditioning &amp; Refrigeration Part 1</b>         |
| <b>BAE613 Mechanical Instrumentation Process</b>                  |
| <b>BAE614 Machine Design</b>                                      |
| <b>BAE512 Building Service Water Supply System</b>                |
| <b>BAE511 Air-conditioning &amp; Refrigeration Part 2</b>         |
| <b>BAE613 Mechanical Instrumentation Process</b>                  |
|   |

**Year (4) Part 1 BE (Mechanical + General Related Subjects)**

|   |
|---|
| <b>BAE 601 Computer Programming</b>                                     |
| <b>BAE 602 Computer Network</b>   |
| <b>BAE 603 Software Engineering</b>                                     |
| <b>BAE 605 Engineering Management</b>                                   |
| <b>BAE 606 Building Service Electrical &amp; Mechanical Engineering</b> |

**Year (4) Part 2**

**Bachelor of Engineering (Mechanical) Specialization ( 13 pt)**

BAE311 Plant Engineering (2 pt)

BAE312 Design Engineering (2 pt)

BAE313 Environmental Control (2 pt)

BAE314 Mechanical Power Generation (2 pt)

BAE315 Materials Engineering (2 pt) Part 1 Part 2

BAE 608 Engineering Competency Demonstration Report Writing (3 pt)

**Elective (2 pt)**

| Subjects                       |
|--------------------------------|
| BAE513 Production Technology   |
| BAE611 Maintenance Engineering |
| BAE612 Engineering Metallurgy  |

Bachelor of Engineering (Civil-Building Services)

STAGE (3) BASIC ELECTRICAL & ELECTRONICS ENGINEERING ( 18 Pt)

REFER DIPLOMA/ADVANCED DIPLOMA IN ELECTRICAL ENGINEERING DETAILED CONTENTS

EE101 DC Circuit Problems

EE102 Basic Electrical Fitting & Wiring

EE103 Basic Electrical Drafting

EE104 Electrical Equipments Safety Protection

EE105 Electrical Installation Design

EE107 Electrical Equipments

EE106 Advanced Electrical Wiring

EE108 Electrical Fault Finding

EE109 Electrical Control Circuits

EE111 Electromagnetism & Basic Electrical Machines

EE112 Alternating Current Principle

EE113 Electrical Fundamental

EE115 Basic Analogue & Digital Electronics

EE116 Process Control System

EE117 Solar Electrical System

EE119 Electrical Risk Assessment

EE120 Electrical Contracting & Specifications

EE308 Sustainability

**STAGE (4 A) ADVANCED MECHANICAL ENGINEERING STUDY ( 6Pt)**

**REFER DIPLOMA/ADVANCED DIPLOMA IN MECHANICAL ENGINEERING DETAILED CONTENTS**

ME 102 Engineering Thermodynamics

ME 109 Engineering Drawing

ME 107 Heat Transfer

ME 201 Introduction to Fluid Mechanics

ME 204 Engineering Fluid Mechanics

ME 301 Fluid Dynamics

**STAGE (4B)ADVANCED ELECTRICAL & ELECTRONICS ENGINEERING STUDY**

**(ADVANCED DIPLOMA) ( 4 pt)**

**REFER DIPLOMA/ADVANCED DIPLOMA IN ELECTRICAL ENGINEERING DETAILED CONTENTS**

EE201 Engineering Mathematics

EE204 Engineering Physics

EE302 Advanced Engineering Mathematics

EE307 Energy Efficient Building Design

**STAGE (5)BACHELOR OF APPLIED ENGINEERING (BUILDING SERVICE) DEGREE ( 32 pt)**

|   |
|---|
| <b>Subjects</b>   |
| <b>BAE 401 Advanced Engineering Mathematics</b>           |
| <b>BAE 402 Calculus</b>                                   |
| <b>BAE 403 Engineering Mechanics</b>                      |
| <b>BAE 404 Engineering Materials &amp; Thermodynamics</b> |

|   |
|---|
| <b>BAE 508 Industrial Engineering &amp; Industrial Management</b>       |
| <b>BAE 601 Computer Programming</b>                                     |
| <b>BAE 605 Engineering Management</b>                                   |
| <b>BAE 606 Building Service Electrical &amp; Mechanical Engineering</b> |
| <b>BAE 609 Design Project</b>   |

**Bachelor of Engineering (Mechanical-Mechatronics)**

**Advanced Diploma of Mechanical Engineering)**

REFER DIPLOMA/ADVANCED DIPLOMA IN ELECTRICAL ENGINEERING DETAILED CONTENTS

REFER DIPLOMA/ADVANCED DIPLOMA IN MECHANICAL ENGINEERING DETAILED CONTENTS

**(1) ME104** Principle of Machine

(2)EE624 Process Control

**EE115 Basic Analogue & Digital Electronics**

**EE116 Process Control System**

(3)ME 334 Airconditioning and Refrigeration

(4) ME202 Aerodynamics

(5) ME 302 Automation-and-Robotics

(6) ME 303 Computer Aided Design and Manufacturing

(7) ME 234 Wind Turbines

(8) ME 201 Introduction to Fluid Mechanics

(9) ME 204 Engineering Fluid Mechanics +  
ME 301 Fluid Dynamics

(10) ME 206 Introduction to Turbo Machinery

(11)ME 205 Manufacturing Processes & Materials

- (12) ME 207 Chemical Thermodynamics
- (13) ME 208 Hydrocarbons
- (14) ME 634 Pneumatics
- (15) ME 203 Control
- (16) ME 534 Numerical Control
- (17) ME 434 Mechnronics-Robotics
- (18) EE 617 Building Electrical and Mechanical System
- (19) EE105 Electrical Installation Design  
EE107 Electrical Equipments

### EE105 Electrical Installation Design

### EE107 Electrical Equipments

- (20) EE106 Advanced Electrical Wiring
- (21) EE116 Process Control
- (22) EE117 Solar Electrical System
- (23) EE119 Electrical Risk Assessment  
EE120 Electrical Contracting
- (24) ME 109 Engineering Drawing  
EE301 Advanced Electrical Drafting
- (25) EE121 Electronics Power Control Devices
- (26) EE206 AC
- (27) EE207 DC
- (28) EE202 Electrical Circuits
- (29) EE203 Three Phase Power Circuits

- (30) ME 305 Corrosion Prevention
- (31) ME 306 Theory-of-waves-in- materials



## Bachelor of Applied Engineering (Mechanical-Mechatronics)

|   |
|---|
| <b>Subjects</b>   |
| <b>BAE 401 Advanced Engineering Mathematics</b>                         |
| <b>BAE 402 Calculus</b>   |
| <b>BAE 403 Engineering Mechanics</b>                                    |
| <b>BAE 404 Engineering Materials &amp; Thermodynamics</b>               |
| <b>BAE 405 Advanced Circuit Analysis</b>                                |
| <b>BAE 406 Electro-mechanics</b>  |
| <b>BAE 408 Analogue &amp; Digital Electronics</b>                       |
| <b>BAE 502 Linear System</b>  |
| <b>BAE 503 Control System</b>   |
| <b>BAE 507 Electro-mechanical Energy Conversion</b>                     |
| <b>BAE 508 Industrial Engineering &amp; Industrial Management</b>       |
| <b>BAE 601 Computer Programming</b>                                     |
| <b>BAE 602 Computer Network</b>   |
| <b>BAE 603 Software Engineering</b>                                     |
| <b>BAE 604 Telecommunication Engineering</b>                            |
| <b>BAE 605 Engineering Management</b>                                   |
| <b>BAE 606 Building Service Electrical &amp; Mechanical Engineering</b> |

### **Diploma in Mechanical /Automotive Engineering Study Program**

#### DIP ME/AE Part 1

#### Month – 1 (Week 1+2)

Study EE101 Powerpoints

## EE101 DC Circuit Problems

### TUTORING LESSONS

[Lesson 1](#) [Lesson 2](#) [Lesson 3](#)

#### Test & Assessment

[http://www.filefactory.com/file/58r3nfe1qieh/n/E003\\_E004\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/58r3nfe1qieh/n/E003_E004_Online_Test_1_Question_pdf)

[http://www.filefactory.com/file/796n6fdurdij/n/E003\\_E004\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/796n6fdurdij/n/E003_E004_Online_Test_1_Answer_doc)

Do the tests and send the answer sheet in soft copy by e-mail to [iqytechnicalcollege@gmail.com](mailto:iqytechnicalcollege@gmail.com)

Then do the following test

#### **E003+E004 Online test**

Ref 1

Four resistors 1 ohm, 2 ohm , 3 ohm and 4 ohm are connected in series to 5V. Calculate the circuit current & potential difference across each resistor.

|        |                |   |                      |
|--------|----------------|---|----------------------|
| A      | 1A,3V,2V,5V,7V | B | 0.5A,0.5V,1V,1.5V,2V |
| C      | 3A,1V,5V,6V,7V | D | 0.A,1V,2V,3V,4V      |
| Answer |                |   |                      |

Ref 2

A 2.2K  $\Omega$  resistor is connected in series with a resistor of unknown value across 16V supply. If the current is 5 mA, calculate the value of unknown resistor.

|        |              |   |              |
|--------|--------------|---|--------------|
| A      | 2 K $\Omega$ | B | 3 K $\Omega$ |
| C      | 4 K $\Omega$ | D | 1 K $\Omega$ |
| Answer |              |   |              |

Ref 3

Two resistors are connected in series to a 115V supply, one is known to have  $470\ \Omega$  and voltage across it is 47V. Calculate (a) the value of second resistor (b) the circuit current.

|        |                            |   |                             |
|--------|----------------------------|---|-----------------------------|
| A      | $680\ \Omega, 0.1\text{A}$ | B | $800\ \Omega, 0.2\text{A}$  |
| C      | $100\ \Omega, 1\text{A}$   | D | $1200\ \Omega, 0.1\text{A}$ |
| Answer |                            |   |                             |

Ref 4

Resistors of  $5\ \Omega$ ,  $10\ \Omega$  and  $3\ \Omega$  are connected in parallel to 12V supply. Calculate the supply current.

|        |    |   |    |
|--------|----|---|----|
| A      | 2A | B | 3A |
| C      | 1A | D | 4A |
| Answer |    |   |    |

Ref 5

Resistors of  $33\text{K}\ \Omega$ , and  $68\ \text{K}\ \Omega$  are connected in parallel to 50V. Calculate (a) total circuit resistance (b) total circuit current (c) individual branch currents.

|        |  |   |  |
|--------|--|---|--|
| A      | $44.5\ \text{K}\ \Omega, 4.5\text{mA}, 3\text{mA}, 1.58\text{mA}$    | B | $30\ \text{K}\ \Omega, 3\text{mA}, 2\text{mA}, 1\text{mA}$ |
| C      | $22.2\ \text{K}\ \Omega, 2.25\text{mA}, 1.5\text{mA}, 0.79\text{mA}$ | D | $60\ \text{K}\ \Omega, 6\text{mA}, 4\text{mA}, 2\text{mA}$ |
| Answer |  |   |  |


Ref 6

Resistors of values  $12\ \Omega$  and  $8\ \Omega$  are connected in parallel with  $R_3$  of unknown value across a 6V supply. When the current from the supply is 2.25A, calculate (a) the value of  $R_3$  (b) current flowing in  $R_3$ .

|        |                            |   |                           |
|--------|----------------------------|---|---------------------------|
| A      | $6\ \Omega, 1\text{A}$     | B | $12\ \Omega, 0.5\text{A}$ |
| C      | $24\ \Omega, 0.25\text{A}$ | D | $8\ \Omega, 1.25\text{A}$ |
| Answer |                            |   |                           |

Ref 7

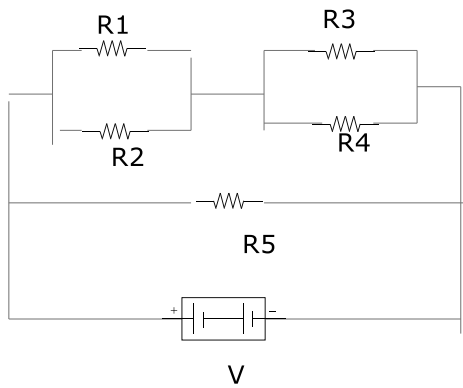Five resistors are connected as follows. Find (a)  $R_t$  (b)  $I_t$  (c)  $2\ \Omega$  resistor current.



$R1=2\ \Omega$ ,  $R2=8\ \Omega$ ,  $R3=3\ \Omega$ ,  $R4=6\ \Omega$ ,  $R5=7.2\ \Omega$ .  $V=6\text{V}$

|               |                            |   |                         |
|---------------|----------------------------|---|-------------------------|
| A             | 3.6 $\Omega$ , 5A, 2.66A   | B | 4.8 $\Omega$ , 5A, 7A   |
| C             | 2.4 $\Omega$ , 2.5A, 1.33A | D | 7.2 $\Omega$ , 7.5A, 4A |
| <b>Answer</b> |                            |   |                         |

Ref 8

Resistors 1.8 K $\Omega$  and 1.2 K $\Omega$  are connected in series to 12V supply. Calculate the power dissipated in each resistor and total power.

|               |                        |   |                        |
|---------------|------------------------|---|------------------------|
| A             | 0.0288W,0.0192W,0.048W | B | 0.0576W,0.0384W,0.096W |
| C             | 0.0144W,0.009W,0.024W  | D | 1W,0.5W,0.7W           |
| <b>Answer</b> |                        |   |                        |

Ref 9

A 1  $\Omega$  resistor is connected in series with parallel combination of 6  $\Omega$  and 3  $\Omega$  resistors to 6V supply. Calculate (a)  $R_t$  (b) Each resistor current.

|               |                               |   |                               |
|---------------|-------------------------------|---|-------------------------------|
| A             | 6 $\Omega$ , 1A, 1.32A, 2.66A | B | 4 $\Omega$ , 1A, 2A, 3A       |
| C             | 10 $\Omega$ , 4A, 3A, 5A      | D | 3 $\Omega$ , 2A, 0.66A, 1.33A |
| <b>Answer</b> |                               |   |                               |

Ref 10

Resistors of 2.2K  $\Omega$  and 7.88K  $\Omega$  are connected in series and parallel across 3.3K  $\Omega$  and 2.7K  $\Omega$  series combination. They are connected to 9V supply .Calculate (a)  $R_t$  (b)  $I_t$  (c) Each resistor current.

|        |                                    |   |                                 |
|--------|------------------------------------|---|---------------------------------|
| A      | 3.75K $\Omega$ , 2.4mA,0.9mA,1.5mA | B | 7.5K $\Omega$ , 4.8mA,1.8mA,3mA |
| C      | 2K $\Omega$ , 1.2mA,0.5mA,1mA      | D | 10K $\Omega$ , 8mA,2mA,3mA      |
| Answer |                                    |   |                                 |

Ref 11

3 filament lamp indicators are each rated 12V and 0.36 w. If they are connected in series, what supply voltage should be used? Find supply voltage, the current and total power dissipated.

|        |                 |   |                  |
|--------|-----------------|---|------------------|
| A      | 72V,0.06A,2.16W | B | 108V,0.09A,3.24W |
| C      | 36V,0.03A,108W  | D | 18V,0.015A,0.54W |
| Answer |                 |   |                  |

Ref 12


A circuit is fed with a 9V supply but a 4V ground potential is required at the base of a transistor. If this voltage is to be derived from 12 K $\Omega$  resistor connected to ground. Calculate the value of second resistor forming potential divider.

|        |              |   |              |
|--------|--------------|---|--------------|
| A      | 30K $\Omega$ | B | 20K $\Omega$ |
| C      | 15K $\Omega$ | D | 5K $\Omega$  |
| Answer |              |   |              |

Ref 13

Find RX

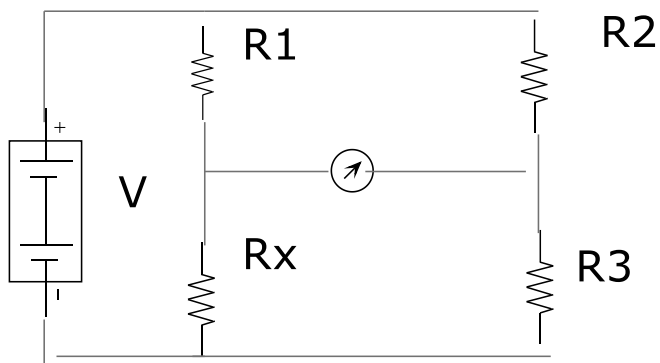If  $R_1=1000 \Omega$ ,  $R_2=1000 \Omega$ ,  $R_3=2715 \Omega$ ,  $V= 1.5V$  at bridge balanced condition.



|        |               |   |               |
|--------|---------------|---|---------------|
| A      | 2715 $\Omega$ | B | 3000 $\Omega$ |
| C      | 1000 $\Omega$ | D | 2000 $\Omega$ |
| Answer |               |   |               |

Ref 15

A cell has emf 1.5V and internal resistance 0.5 ohm. Calculate its terminal voltage at (a) No load (b) providing 200mA current (c) when connected to a load of 8 ohm.

|        |                |   |                   |
|--------|----------------|---|-------------------|
| A      | 3V, 2.8V, 2.8V | B | 1.5V, 1.4V, 1.41V |
| C      | 6V, 1.4V, 1.4V | D | 3V, 1.4V, 1.41V   |
| Answer |                |   |                   |

Ref 16

A battery is made by connection 8 cells in series. Each has 1.5V and internal resistance 0.35 ohm. Calculate (a) EMF & internal resistance of battery. (b) The terminal voltage when supplying 400mA. (c) The current & terminal voltage when a load of resistance 20 ohm is connected to battery.

|        |                            |   |                           |
|--------|----------------------------|---|---------------------------|
| A      | 12V, 2.8 $\Omega$ , 10.11V | B | 15V, 1.4 $\Omega$ , 5.1V  |
| C      | 12V, 2.8 $\Omega$ , 5.1V   | D | 6V, 2.8 $\Omega$ , 10.11V |
| Answer |                            |   |                           |

**SUBMIT THE SCANNED COPY OF ANSWER to**

**Dr Kyaw Naing**

**PO BOX 227**

**Marrickville, NSW 1475, Sydney, Australia**

## Month – 1 (Week 3+4)

Study EE102 Powerpoints

### EE102 Basic Electrical Fitting & Wiring

#### TUTORING LESSONS

[Lesson 1](#) [Lesson 2](#) [Lesson 3](#)

#### Test & Assessment

<http://www.classroomclipboard.com/503511/Home/Test/e3b8ef2c72e94d209034f9633e22c26a#/InitializeTest.xaml>

Type your name Put the following access code

CEAHU

Then do the following test

Study EE102 & then do the following Exercises

## EE102 Exercises

Q1

Ref 575

The tests to be conducted for electrical installation safety are

---

- Earthing system test
- Insulation resistance test

Polarity test

All above

Q2

Ref 574

The insulation resistance must be

---

very high

very low

Q3

Ref 573

The resistance of earth must be less than

---

2 ohm

10 ohm

20 ohm

Q4

Ref 572

The switch should be connected on

Q5



Ref 571

The colour of earth wire is

---

- Red
- Black
- Green and yellow

Q6

Ref 570

The colour of neutral wire is

---

- Black
- White
- Green

Q7

Ref 569

The colours of active wire are

---

- Red
- Blue
- Black
- Brown

First and last one

Q8

Ref 568

Two types of failure of fixing are

Q9

Ref 567

How many nails should be driven into each brick

---

One

Two

Three

Q10

Ref 566

Nail should not be driven into mortar joint

---

True

False

Q11

Ref 565

To drill the hole, a pilot hole must have

---

- The same diameter as to the hole that you want to drill
- Smaller diameter as to the hole that you want to drill
- Bigger diameter as to the hole that you want to drill

Q12

Ref 564

It is safe to remove the person who is electrocuted at 1000V

---

- True
- False

Q13

Ref 563

To use the hand held electrical equipments in the workplace, the insulation must be

---

- Double insulation
- Single insulation

Q14

Ref 562

It is safe to walk in forklift way in the factory and stand under the scaffolding

---

- True
- False

Q15

Ref 561

To lift a heavy equipments

---

- Bend the kneel and lift with kneel force
- Bend the back and simply lift it

Q16

Ref 560

Safety glass and safety hat are included in

Q19

Ref 559

Employer will not need to take any responsibility to provide the safe operational equipments in the workplace

---

- True
- False

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

## Month – 2 (Week 1+2)

Study EE104 Powerpoints

### TUTORING LESSONS

#### EE104 Electrical Equipments Safety Protection

##### Lesson 1

Then do the following test

#### EE104 Electrical Equipments Safety Protection

Study the notes in EE104 Power Points & do the following exercises.

Q1. Sketch RCD Connection

Q2. Sketch earthing system and earthing arrangement.

Q3. What is the supplementary system for earthing?

Q4. What are the types of earthing systems?

Q5. Sketch the connection diagram for smoke alarm.

Q6. Why earthing system is provided?

Q7. Sketch the arrangement of an earthing system.

Q8. Write the formula to calculate the voltage drop.

Q9. How will you isolate the live parts?

Q10.What is the meaning of ELCBN

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

## Month – 2 (Week 3+4)

Study EE111 Powerpoints

### EE111 Electromagnetism & Basic Electrical Machines

#### TUTORING LESSONS

##### Lesson 1

##### Test & Assessment

[http://www.filefactory.com/file/7c658zyrj9gx/n/G001\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/7c658zyrj9gx/n/G001_Online_Test_1_Question_pdf)

[http://www.filefactory.com/file/1h8minstf7ux/n/G001\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/1h8minstf7ux/n/G001_Online_Test_1_Answer_doc)

Then do the following test

### EE111 Electromagnetism & Basic Electrical Machines

Study the notes

And do the following exercises.

#### G001 Online Test

Ref137

The flux is equal to

|   |                    |   |                         |
|---|--------------------|---|-------------------------|
| A | $\phi = F_m / R_m$ | B | $\phi = F_m \times R_m$ |
| C | $\phi = R_m / F_m$ | D | $\phi = F_m + R_m$      |

|        |  |
|--------|--|
| Answer |  |
|--------|--|

Ref 138

Rm is equal to

|        |            |   |           |
|--------|------------|---|-----------|
| A      | $l\mu / A$ | B | $L/\mu A$ |
| C      | $L\mu A$   | D | $\mu A/l$ |
| Answer |            |   |           |

Ref139

Flux density is equal to

|        |          |   |           |
|--------|----------|---|-----------|
| A      | $\phi A$ | B | $A/ \phi$ |
| C      | $\phi/A$ | D | $\Phi+A$  |
| Answer |          |   |           |

Ref140

The torque produced in electric motor is equal to

|        |             |   |              |
|--------|-------------|---|--------------|
| A      | $T = BL r$  | B | $T = Br/ L$  |
| C      | $T = BL/ r$ | D | $T + Br + L$ |
| Answer |             |   |              |

Ref141

A plunger brake electro-magnetic operates at a flux density of 12 tesla. If the CSA of the magnetic circuit is 0.04 sq-m and reluctance is 12000 amp-turn / wb, what current is required to operate the magnet if the coil has 1000 turns.

|        |        |   |        |
|--------|--------|---|--------|
| A      | 0.288A | B | 0.576A |
| C      | 1.3A   | D | 2.8A   |
| Answer |        |   |        |

Ref142

The induced voltage in conductor moving in magnetic field is

|        |                      |   |                      |
|--------|----------------------|---|----------------------|
| A      | $E = BLV \sin\Theta$ | B | $E = BLV \cos\Theta$ |
| C      | $E = BLV$            | D | $E = Bl \sin\Theta$  |
| Answer |                      |   |                      |

Ref143

The voltage induced in coil of N turns is

|        |                            |   |                |
|--------|----------------------------|---|----------------|
| A      | $V = N \phi$               | B | $V = NI$       |
| C      | $V = N \times d \phi / dt$ | D | $V = N^2 \phi$ |
| Answer |                            |   |                |

Ref144

What is the velocity of a conductor 150 mm long and moving at right angle to magnetic field having a flux density of 0.4 tesla? The induced voltage is 4V.

|        |        |   |         |
|--------|--------|---|---------|
| A      | 6 m/s  | B | 1.5 m/s |
| C      | 12 m/s | D | 3.3 m/s |
| Answer |        |   |         |

Ref145

The force between two current carrying conductors is

|        |                              |   |                           |
|--------|------------------------------|---|---------------------------|
| A      | $F = 10^{-7} I / d$          | B | $F = NI / d$              |
| C      | $F = 2 \times 10^{-7} I / d$ | D | $F = 4 \pi 10^{-7} I / d$ |
| Answer |                              |   |                           |

Ref146

A transformer has 50 turns on the primary and 600 turns on secondary . If a flux of 0.25 wb is induced to zero in 10 ms, calculate the induced emf in each coil.

|   |                            |   |                             |
|---|----------------------------|---|-----------------------------|
| A | $E_1 = 250V, E_2 = 3000V$  | B | $E_1 = 2500V, E_2 = 30000V$ |
| C | $E_1 = 300V, E_2 = 25000V$ | D | $E_1 = E_2 = 3000V$         |



|        |  |
|--------|--|
| Answer |  |
|--------|--|

Ref147

If a conductor is being rotated at 2000 RPM in magnetic field and induces 400V . If it is rotated at 1000 RPM.. Find the induced emf.

|        |      |   |      |
|--------|------|---|------|
| A      | 100V | B | 200V |
| C      | 400V | D | 50V  |
| Answer |      |   |      |

Ref148

A 240 V coil 5000T produces magnetizing force 4000AT/ m . The magnetic circuit is 200 mm long. CSA 500 sq-mm. Find the resistance of the coil.

|        |       |   |       |
|--------|-------|---|-------|
| A      | 1500Ω | B | 3000Ω |
| C      | 750Ω  | D | 150Ω  |
| Answer |       |   |       |

**SUBMIT THE SCANNED COPY OF ANSWER to**

**Dr Kyaw Naing**

**PO BOX 227**

**Marrickville, NSW 1475, Sydney, Australia**

**Month – 3 (Week 1+2)**

**Study EE112 Powerpoints**

**EE112 Alternating Current Principle**

**TUTORING LESSONS**

[Lesson 1](#)   [Lesson 2](#)

**Test & Assessment**

[http://www.filefactory.com/file/7ebmnciqxmf3/n/G002\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/7ebmnciqxmf3/n/G002_Online_Test_1_Question_pdf)

[http://www.filefactory.com/file/6d3yokhjziur/n/G002\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/6d3yokhjziur/n/G002_Online_Test_1_Answer_doc)

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

Password- [iqytechnicalcollege](#)

And do the following exercises.

Then do the following test

### EE112 Alternating Current Principle

Study Power point Part 1 & 2

And do the following exercises.

#### G002 Online Test

Ref149

A sine wave voltage of 240V RMS is applied to a resistive circuit of 60Ω. Calculate (a) RMS value of current (b) Maximum value of current.

|        |          |   |           |
|--------|----------|---|-----------|
| A      | 2A, 4A   | B | 4A, 5.65A |
| C      | 2A, 2.8A | D | 1A, 2A    |
| Answer |          |   |           |

Ref150

A coil of negligible resistance draws a current of 0.2A (RMS) when connected to 240V, 50HZ.

(a) Determine inductive reactance (b) Coil inductance.

|        |               |   |               |
|--------|---------------|---|---------------|
| A      | 600Ω , 3.8 H  | B | 1200Ω , 1.9 H |
| C      | 1200Ω , 3.8 H | D | 1800Ω , 7.6 H |
| Answer |               |   |               |

Ref151

A 64 mH inductor is connected in series with a 300Ω resistor to a 1000HZ AC supply voltage of 10V rms. Find (a) the impedance (b) The phase angle (c) The current (d) the potential drop across resistor.

|        |   |   |   |
|--------|---|---|---|
| A      | 500Ω ,( 53.2 Deg),<br>0.002A (-53.2Deg),<br>6V,8V | B | 500Ω ,( 36.8 Deg),<br>0.001A (+53.2Deg),<br>8V,6V |
| C      | 500Ω ,( 0 Deg),<br>0.002A (-0 Deg),<br>6V,8V      | D | 500Ω ,( 90 Deg),<br>0.002A (-90 Deg),<br>6V,8V    |
| Answer |   |   |   |

Ref152

Find the current in the circuit when an AC voltage 10V rms at 1000HZ is applied to 2 μF capacitor.

|        |        |   |       |
|--------|--------|---|-------|
| A      | 0.375A | B | 0.25A |
| C      | 0.125A | D | 0.5A  |
| Answer |        |   |       |

Ref153

A 1 μF capacitor is connected in series with 200 Ω resistor to 10V rms. 1600HZ supply. Find (a) the impedance (b) The phase angle (c) The current (d) Potential drop across resistor (e) Potential drop across capacitor.

|               |   |   |   |
|---------------|---|---|---|
| A             | 111.3 $\Omega$ ,(-26.5 Deg),<br>0.0224A (-26.5Deg),<br>4.5V,2.24V | B | 222.6 $\Omega$ ,( +26.5 Deg),<br>0.0224A (-26.5Deg),<br>9V ,4.48V |
| C             | 222.6 $\Omega$ ,( 0 Deg),<br>0.0224A (0 Deg),<br>9V ,4.48V        | D | 222.6 $\Omega$ ,( -26.5 Deg),<br>0.0448A (+26.5Deg),<br>9V ,4.48V |
| <b>Answer</b> |   |   |   |

Ref154


A series circuit is connected to a 10V rms AC supply. The circuit has resistance 100  $\Omega$ , inductive reactance 300  $\Omega$ , capacitive reactance 400  $\Omega$ . Find (a) Impedance (b) Current (c) Phase angle (d) Voltage drop across resistor (e) Voltage drop across inductor (f) Voltage drop across capacitor.

|               |  |   |   |
|---------------|--|---|---|
| A             | 141 $\Omega$ (Angle -45 Deg), 0.071A, 45 Deg,<br>7.1V, 21.3V,28.4V | B | 70.7 $\Omega$ (Angle +45 Deg), 0.035A, 45 Deg,<br>3.35V, 10.65V,14.2V |
| C             | 141 $\Omega$ (Angle 45 Deg), 0.071A,-45 Deg<br>7.1V, 28.4V, 21.3V  | D | 141 $\Omega$ (Angle 0 Deg),0.071A, 0 Deg,<br>7.1V, 21.3V, 28.4V       |
| <b>Answer</b> |  |   |   |

Ref155

The following is a diagram of a parallel circuit with a supply voltage 100V rms at 50Hz. Determine the followings.

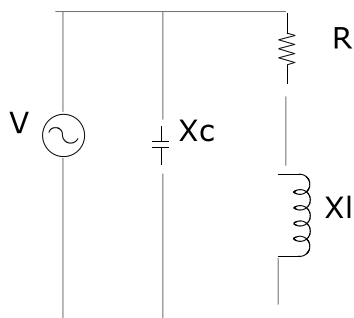(a) Total circuit current (b) Total circuit impedance (c) Phase angle between circuit current and applied voltage (d) Power factor of circuit.



$X_c = 318.5 \Omega$ ,  $R = 100 \Omega$ ,  $X_l = 94.2 \Omega$ ,  $V = 100 \text{ V}$ , 50Hz

|   |  |   |  |
|---|--|---|--|
| A | 1.8A (Angle -36.8 Deg), 206 $\Omega$ , 56.86 Deg,<br>0.8 | B | 0.97A (Angle +36.8 Deg), 103 $\Omega$ , 36.8 Deg<br>0.59 |
|---|--|---|--|

|        |   |   |   |
|--------|---|---|---|
| C      | 0.97A (Angle -36.8 Deg),103 $\Omega$ , 36.8 Deg<br>0.59 | D | 0.97A (Angle +53.2 Deg),206 $\Omega$ , 53.2 Deg<br>0.59 |
| Answer |   |   |   |

Ref156

A capacitor draws 0.971 Amp at PF 0.34 from 100V supply. Total power is

|        |        |   |        |
|--------|--------|---|--------|
| A      | 36.8W  | B | 100W   |
| C      | 52.43W | D | 70.7 W |
| Answer |        |   |        |

Ref157

The phase voltage and current in 3 phase star connected current are 240V and 50A. Find the line voltage and line current.

|        |                 |   |                 |
|--------|-----------------|---|-----------------|
| A      | 415V rms, 50A   | B | 240V rms, 50A   |
| C      | 415V rms, 86.5A | D | 240V rms, 86.5A |
| Answer |                 |   |                 |

Ref158

A delta connected load takes a line current 40A and line voltage 415V. Find (a) Phase current (b) Phase voltage

|        |           |   |             |
|--------|-----------|---|-------------|
| A      | 40A, 415V | B | 23.1A, 415V |
| C      | 40A, 240V | D | 23.1A. 240V |
| Answer |           |   |             |

Ref159

Three phase 415V, 37.3 KW, Delta connected alternator has efficiency 90% and PF 0.88 Lagging. Find (a) Line current (b) Phase current.

|               |              |   |               |
|---------------|--------------|---|---------------|
| A             | 130A, 75.6A  | B | 65.5 A, 75.6A |
| C             | 65.5A, 37.8A | D | 130A, 37.8A   |
| <b>Answer</b> |              |   |               |

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

## Month – 3 (Week 1+2)

Study EE201Powerpoints

### EE201 Engineering Mathematics

#### TUTORING LESSONS

[EE201 Part 1](#) [EE201 Part 2](#) [EE201 Part 3](#) [EE201 Part 4](#)

#### Test & Assessment

[http://www.filefactory.com/file/5ho7s6h0svhv/n/E050\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/5ho7s6h0svhv/n/E050_Online_Test_1_Answer_doc)

[http://www.filefactory.com/file/6dqp87kdsorz/n/E050\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/6dqp87kdsorz/n/E050_Online_Test_1_Question_pdf)

Password- **iqytechnicalcollege**

Then do the following test. Download from the given link

E050 MCQ Practice 1

[http://www.filefactory.com/file/6dqp87kdsorz/n/E050\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/6dqp87kdsorz/n/E050_Online_Test_1_Question_pdf)

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

## Month – 3 (Week 3+4)

Study EE204 Powerpoints

### EE204 Engineering Physics

#### TUTORING LESSONS

[EE204 Part 1](#) [EE204 Part 2](#) [EE204 Part 3](#) [EE204 Part 4](#) [EE204 Part 5](#)

[EE204 Part 6](#)

#### Test & Assessment

[http://www.filefactory.com/file/13o82qnudgr3/n/E046\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/13o82qnudgr3/n/E046_Online_Test_1_Question_pdf)

[http://www.filefactory.com/file/6o2lsbtqe7tt/n/E046\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/6o2lsbtqe7tt/n/E046_Online_Test_1_Answer_doc)

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

Password- [iqytechnicalcollege](#)

Then do the following test. Download from the given link

#### E046 Online Test

Ref66

The car is driven along a straight road for 8.4 Km at 70 Km/ hr. At which point the truck runs off the gasoline & stops. The next 30 minutes, the driver walks along the road for another 3 Km.

(a) What is over all displacement?

(b)What is time interval from the beginning of the drive to arrival at the station?

(c)What is average velocity?

|        |                              |   |                        |
|--------|------------------------------|---|------------------------|
| A      | 20 km, 1 HR, 20 km/hr        | B | 30 km, 2 HR, 30 km /hr |
| C      | 10.4 km, 0.62 HR, 16.8 km/hr | D | 50 km, 5 HR, 70 km/hr  |
| Answer |                              |   |                        |

Ref70

On a hot day in Las Vegas, an oil tanker loaded 37000 L of diesel fuel. It encounters cold weather on Utah where temperature was 23 Degree K lower than in Las Vegas. How many litres did it deliver?

Volume expansion for diesel fuel is  $9.5 \times 10^{-4}$  / Deg C coefficient of linear expansion is  $11 \times 10^{-6}$  /deg c

|        |         |   |         |
|--------|---------|---|---------|
| A      | 18380 L | B | 36190 L |
| C      | 20000 L | D | 10000 L |
| Answer |         |   |         |

Ref73

A cylinder contains 12 L of oxygen at 20 deg C and 15 atm. The temperature is raised to 35 deg C and the volume is reduced to 8.5L . What is the final pressure of the gas in atmosphere.?

|        |        |   |        |
|--------|--------|---|--------|
| A      | 22 atm | B | 33 atm |
| C      | 11 atm | D | 44 atm |
| Answer |        |   |        |

Ref76

Three Carnot engines operate between reservoir temperatures of (a) 400 deg K and 500 deg K (b) 600 and 800 deg K (c) 400 and 600 deg K. rank the engineers according to thermal efficiencies. Greatest first.



|        |         |   |         |
|--------|---------|---|---------|
| A      | c, b, a | B | a, b, c |
| C      | b, c, a | D | Equal   |
| Answer |         |   |         |

Ref79

At  $t = 0$ , the displacement  $X(0)$  of the block is  $-8.5$  cm. The block's velocity  $V(0)$  is  $-0.92$  m/s and its acceleration  $a(0)$  is  $47$  m/s<sup>2</sup>

- (a) What is the angular velocity  $\omega$  of this system?  
 (b) What are the phase constant  $\phi$  and amplitude  $X_m$  ?

|        |                             |   |                         |
|--------|-----------------------------|---|-------------------------|
| A      | 22.5 rad/s, 155 deg, 9.4 cm | B | 50 rad/s, 30 deg, 18 cm |
| C      | 100 rad/s, 45 deg, 10 m     | D | 15 rad/s, 75 deg, 4cm   |
| Answer |                             |   |                         |

Ref82

The following equations give the position  $X(t)$  of a particle in four situations

(a)  $X = 8t - 4$  (b)  $x = -6t^3 + 9t^2 + 6$  (c)  $X = 3/t^2 - 9/t$  (d)  $X = 7t^2 - 4$  To which of these situations? Do the constant acceleration formulae apply?

|        |   |   |   |
|--------|---|---|---|
| A      | a | B | b |
| C      | c | D | d |
| Answer |   |   |   |

Ref85

$$a = 3i - 8j \quad b = -2i + 4j \quad c = -4j$$

Find the resultant vector for  $a+b+c$

|        |               |   |           |
|--------|---------------|---|-----------|
| A      | $10i + 2j$    | B | $7i + 5j$ |
| C      | $2.5i - 2.3j$ | D | 0         |
| Answer |               |   |           |

Ref88

2 kg Tin is accelerated at  $3\text{ m/s}^2$  in the direction shown by a over a frictionless horizontal surface. The acceleration is caused by three forces . What is the third force?

|        |     |   |       |
|--------|-----|---|-------|
| A      | 20N | B | 10N   |
| C      | 1N  | D | 12.5N |
| Answer |     |   |       |


Ref91

Suppose that the coefficient of static friction  $\mu$  between the rider's clothing and the canvas is 0.4 and the cylinder radius " R" is 2.1 m.

(a) What minimum speed (V) must the cylinder and the rider have if the rider is not to fall when the floor drops? (b) If the rider's mass is 49 Kg, what is the magnitude of centrifugal force on rider?

|        |                |   |               |
|--------|----------------|---|---------------|
| A      | 7.2 m/s, 1200N | B | 3.6 m/s, 600N |
| C      | 21 m/s, 2000N  | D | 30 m/s, 3000N |
| Answer |                |   |               |


Ref94

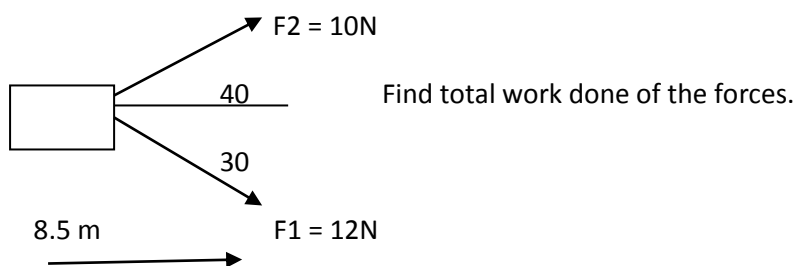

|        |      |   |      |
|--------|------|---|------|
| A      | 306J | B | 153J |
| C      | 469J | D | 73J  |
| Answer |      |   |      |

Ref97

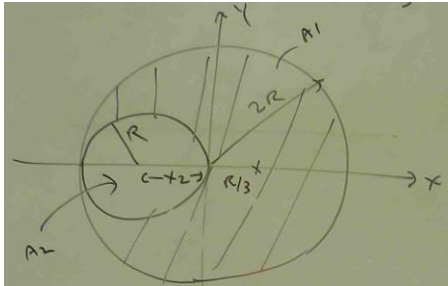The figure shows a uniform metal plate “P” of radius “2R” from which a disk of radius “R” has been stamped out. Using the X-Y co-ordinate system shown, locate the centre of mass of the plate.



|               |                        |   |                      |
|---------------|------------------------|---|----------------------|
| A             | $X_t = R/4, Y_t = R$   | B | $X_t = R, Y_t = R$   |
| C             | $X_t = R/2, Y_t = R/2$ | D | $X_t = R/3, Y_t = 0$ |
| <b>Answer</b> |                        |   |                      |

Ref100

A coach roach rides the rim of a rotating merry go around. If the angular speed is constant, does the coach roach have (a) Radial acceleration ? (b) Tangential acceleration ? What angle  $\Theta_p$  should the arc subtend so that a 15.4 kg at the point “P”.

|               |         |   |         |
|---------------|---------|---|---------|
| A             | 50 Deg  | B | 30 Deg  |
| C             | 111 Deg | D | 200 Deg |
| <b>Answer</b> |         |   |         |


Ref67

A rolling object has linear velocity 342.5 m/s radius =3 m mass =170 kg Calculate total kinetic energy.

|               |                             |   |                           |
|---------------|-----------------------------|---|---------------------------|
| A             | $1.5 \times 10^7 \text{ J}$ | B | $3 \times 10^7 \text{ J}$ |
| C             | $4.5 \times 10^7 \text{ J}$ | D | $6 \times 10^7 \text{ J}$ |
| <b>Answer</b> |                             |   |                           |

Ref68

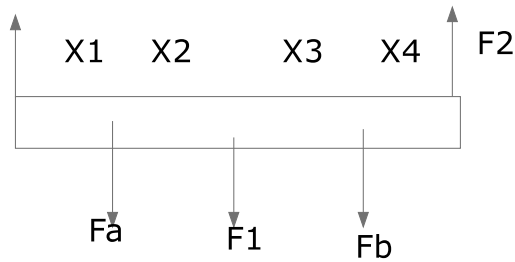The figure gives over view at a uniform rod in static equilibrium , the magnitude of the forces F1 & F2 are



$X1 = 4\text{m}$ ,  $X2 = 2\text{m}$ ,  $X3 = 1\text{m}$ ,  $X4 = 1\text{m}$ ,  $F_a = 10\text{ N}$ ,  $F_b = 30\text{N}$

|               |             |   |                |
|---------------|-------------|---|----------------|
| A             | 90 N, 130 N | B | 22.5 N, 32.5 N |
| C             | 45 N, 65 N  | D | 100 N, 200 N   |
| <b>Answer</b> |             |   |                |

Ref 69

A living room has the floor dimension and height of 3.5 m x 4.2 m. A height of 2.4 m (a) What does the air in the room weigh when the air pressure is 1 atm? (b) What is the magnitude of the atmosphere downward force on the top of your head which we take to have an area of 0.04m<sup>2</sup>

|               |                                 |   |                                  |
|---------------|---------------------------------|---|----------------------------------|
| A             | 420 N, $4 \times 10^3\text{ N}$ | B | 840 N, $8 \times 10^3\text{ N}$  |
| C             | 210 N, $2 \times 10^3\text{ N}$ | D | 1640 N, $6 \times 10^3\text{ N}$ |
| <b>Answer</b> |                                 |   |                                  |

**SUBMIT THE SCANNED COPY OF ANSWER to**

**Dr Kyaw Naing**

**PO BOX 227**

**Marrickville, NSW 1475, Sydney, Australia**

## Month – 3 (Week 3+4)

Study EE208 Powerpoints

### EE208 Operational Amplifiers

#### TUTORING LESSONS

[EE208 Part 1](#) [EE208 Part 2](#) [EE208 Part 3](#)

Password- iqytechnicalcollege

#### Test & Assessment

[http://www.filefactory.com/file/2a3bpimaxqx3/n/H025\\_H045\\_I006\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/2a3bpimaxqx3/n/H025_H045_I006_Online_Test_1_Answer_doc)

[http://www.filefactory.com/file/7j320hlrk6k9/n/H025\\_H045\\_I006\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/7j320hlrk6k9/n/H025_H045_I006_Online_Test_1_Question_pdf)

Password- **iqytechnicalcollege**

**Then do the following test. Download from the given link**

H025 MCQ Practice 1

[http://www.filefactory.com/file/7j320hlrk6k9/n/H025\\_H045\\_I006\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/7j320hlrk6k9/n/H025_H045_I006_Online_Test_1_Question_pdf)

**SUBMIT THE SCANNED COPY OF ANSWER to**

**Dr Kyaw Naing**

**PO BOX 227**

**Marrickville, NSW 1475, Sydney, Australia**

## Month – 4 (Week 1+2)

Study EE209 Powerpoints

### EE209 Analogue Electronics

#### TUTORING LESSONS

[EE209 Part 1](#) [EE209 Part 2](#) [EE209 Part 3](#) [EE209 Part 4](#) [EE209 Part 5](#)

[EE209 Part 6](#) [EE209 Part 7](#)

Password- iqytechnicalcollege

#### Test & Assessment

[http://www.filefactory.com/file/5ht8f5ih8lvr/n/H011\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/5ht8f5ih8lvr/n/H011_Online_Test_1_Answer_doc)

[http://www.filefactory.com/file/74ma7pvjy4un/n/H011\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/74ma7pvjy4un/n/H011_Online_Test_1_Question_pdf)

[http://www.filefactory.com/file/229n33ldqwah/n/H011\\_Online\\_Test\\_2\\_Answer\\_doc](http://www.filefactory.com/file/229n33ldqwah/n/H011_Online_Test_2_Answer_doc)

[http://www.filefactory.com/file/3e54mrgli7ft/n/H011\\_Online\\_Test\\_2\\_Question\\_pdf](http://www.filefactory.com/file/3e54mrgli7ft/n/H011_Online_Test_2_Question_pdf)

**Then do the following test. Download from the given link**

H045 MCQ Practice 1

[http://www.filefactory.com/file/3vpq08cwj73/n/H045\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/3vpq08cwj73/n/H045_Online_Test_1_Question_pdf)

**SUBMIT THE SCANNED COPY OF ANSWER to**

**Dr Kyaw Naing**

**PO BOX 227**

**Marrickville, NSW 1475, Sydney, Australia**

## Month – 4 (Week 3+4)

Study EE302Powerpoints

### EE302 Advanced Engineering Mathematics

#### TUTORING LESSONS

[EE302 Part 1](#)   [EE302 Part 2](#)   [EE302 Part 3](#)   [EE302 Part 4](#)

[http://www.filefactory.com/file/5l9fpcclhjzp/n/E026\\_Online\\_Test\\_3\\_Question\\_pdf](http://www.filefactory.com/file/5l9fpcclhjzp/n/E026_Online_Test_3_Question_pdf)

[http://www.filefactory.com/file/64ccdiuf0ax/n/E026\\_Online\\_Test\\_3\\_Answer\\_doc](http://www.filefactory.com/file/64ccdiuf0ax/n/E026_Online_Test_3_Answer_doc)

Password- iqytechnicalcollege

**Then do the following test. Download from the given link**

E026 MCQ Practice 1

[http://www.filefactory.com/file/68kzit8b851r/n/E026\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/68kzit8b851r/n/E026_Online_Test_1_Question_pdf)

**SUBMIT THE SCANNED COPY OF ANSWER to**

**Dr Kyaw Naing**

**PO BOX 227**

**Marrickville, NSW 1475, Sydney, Australia**

## Month – 5 (Week 1+2)

Study EE309 Powerpoints

**Then do the following exercise**

Write your own experience about establishing a car workshop. It should include

- Business Plan
- Money matter
- Daily operation plan
- Loss/ Profit analysis

- Material Requirement Planning
- Meeting legal requirements.

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

## DIP ME/AE Part 2

### Month – 5 (Week 3+4)

Review the notes in ME 101 Folder

#### TUTORING LESSONS

**ME101 Part 1**

**ME101 Part 2**

Password- iqytechnicalcollege

If you have already done EE201, the point will be given automatically

### Month – 6 (Week 1+2)

#### TUTORING LESSONS

Study ME 102 Powerpoints

**ME102 Part 1**

**ME102 Part 2**

Password- iqytechnicalcollege



**Then do the following exercise**

Study the notes in the YOC-ME102 folder & do the following exercises

Slide 1

Q1. What is thermodynamics system?

Slide 2+3

Q2. Explain the followings

(a) Property (b) Pressure (c) temperature (c) Internal Energy

Slide 4

Q3. Explain the followings

(a) Phase (b) Mixed phase (c) Saturated state (d) Superheated vapour

Slide 5

Q4. Describe the followings

(a) Adiabatic (b) Isothermal (c) Isobaric (d) Isochoric (d) Isentropic (e) Isenthalpic

Slide 6+7

Q5. Write the equation for ideal gas.

Slide 8

Q6. Write the gas equation.

Slide 9

Q7. Write the equation for (a) Constant volume (b) Constant pressure (c) Constant temperature.

Slide 10

Q8. Sketch the Pressure –Volume graphs for

(a) Adiabatic (b) Isothermal (c) Isobaric (d) Isochoric (d) Isentropic (e) Isenthalpic

Slide 11

Q9. Express Van der Waals gas equation of state for gas

Slide 12

Q10. Sketch temperature-enthalpy diagram for Ice, water, Water+ vapour , Vapour

Slide 14.

Q11. Write the equations to calculate steam properties in the mixed region.

Slide 15.

Q12. Write the heat, volume, density of steam equations.

Slide 16

Q13. Self ignition would occur in the engine using certain brand of petrol of the temperature due to compression reached 350 degree C. Calculate the highest ratio of compression that may be used to avoid pre-ignition if the law of compression is.

Slide 18

Q14. Calculate the density of Ethane at 171 bar and 458 deg K , assume for Ethane

$T_e = 305\text{K}$   $P_e = 48.80\text{ bar}$   $R = 319.3\text{ J / Kg K}$  assuming it behaves as a perfect gas.

Slide 21

Q16. Determine the pressure of water vapour at 300 Deg C , if it's specific volume is  $0.2579\text{ m}^3/\text{ kg}$  using the following methods.

(a) Ideal gas equation (b) Van der Waals equation.

## Month – 6 (Week 3+4)

Review the notes in ME 103 Folder

If you have already done EE204, the point will be given automatically

## Month – 7(Week 1+2)

Study ME 108 Powerpoints

### TUTORING LESSONS

#### ME108 Lessons

Password- iqytechnicalcollege

Then do the following exercise

Slide 1+2

Q1. What is internal combustion engine?

Slide 3 to 7

Q2. Explain engine heat transfer.

Slide 8+9

Q3. Explain cylinder heat flux, temperature relation

Slide 10 to 13

Q4. Write gas velocity equation.

Slide 14 to 18

Q5. Write overall heat transfer equation.

Slide 19 to 21

Q6. Explain coolant

Slide 22+23

Q7. Explain the combustion process inside engine.

Slide 25.

Q8. Sketch the strokes of engine.

Slide 28

Q9 Explain thermostat.

Slide 31 +32

Q10. Explain four phases of combustion.

Slide 33

Q11. Describe product of combustion.

Slide 34

Q12. Sketch engine ignition circuit.

Slide 40 to 43

Q13. Explain the followings

(a) Vane pump (b) Diaphragm pump

Slide 44 to 49

Q14. Sketch the followings

(a) Fuel filter (b) Injector

Slide 50

Q15. Explain nozzle

Slide 52

Q16. Copy the diagram on this slide.

Slide 56

Q17. How the engine is stopped?

Slide 57+58

Q18. Explain governor.

Slide 59.

Q19. Explain unit injector system.

Slide 60

Q20. Explain injector operation

**SUBMIT THE SCANNED COPY OF ANSWER to**

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

Month – 7(Week 3+4)

RPL for AE UNITS

AE 101 Auto Diesel+ Auto Electrics

AE 102 Auto General Engine+ Fuel System+ Transmission

AE 103 Engine Assembly +Electrical +Electronics

AE 104 Brake & Steering System

AE 105 Automotive Mechanic

## **COMPLETE DIPLOMA IN MECHANICAL/AUTOMOTIVE ENGINEERING**

The list of the units need to be completed in Advanced Diploma in Mechanical Engineering -Mechatronics (TOTAL 45 pt)

PART (1) (15pt)

**Total points= 45 pt + 30 pt from Dip Automotive Engineering = 75**

**Total points left for degree= 120-75 = 45**

TUTORING LESSONS

## ME104

Password- iqytechnicalcollege

### ME 104 Machine Principle

Study the notes ME 104 Folder and do the following exercises.

Slide 1

Q1. Explain (a) Driving machine (b) Transmission machine

Slide 2 to 4

Q2. Explain driven machine

Slide 5

Q3. What is adjustable mounting?

Slide 6

Q4. Describe the principle of balancing.

Slide 7

Q5. Describe static balancing

Slide 8

Q6. Describe dynamic balancing.

Slide 9

Q7. What are the basic purposes of lubrication.

Slide 10

Q8. Explain the selection of lubricants.

Slide 11+12

Q9 Write the lubricant application process.

Slide 13.

Q10. Describe splash lubrication.

Slide 14.

Q11. What are the characteristics and properties of lubricants?

Slide 15.

Q12. Describe plain bearing.

Slide 16

Q13. Explain journal bearing.

Slide 17+18

Q14.Explain thrust bearing.

Slide 19+20

Q15. Explain linear bearing.

Slide 21 to 23

Q16 Explain ball bearing.

Q17. What is fretting?

Slide 24 to 27

Q18.Describe V belt drive

Slide 28+29

Q19. Explain chain drive

Slide 30+31

Q20. Describe gear drive.

Slide 32+33

Q30 Explain shaft coupling.

Slide 34 to 38

Q31. Explain clutches and method of alignment.

Slide 39 to 42

Q32.Explain O ring.

Slide 43 to 44

Q33.Describe the methods of monitoring the machine conditions.

Slide 45

Q34. What is meant by trouble shooting?

Slide 46+47

Q35. What are the housekeeping procedures in machine repair & maintenance?

ME 108 Principle of Engines

Study the notes in YOC-ME108 Lessons and do the following exercises.

Slide 1+2

Q1. What is internal combustion engine?

Slide 3 to 7

Q2. Explain engine heat transfer.

Slide 8+9

Q3. Explain cylinder heat flux, temperature relation

Slide 10 to 13

Q4. Write gas velocity equation.

Slide 14 to 18

Q5. Write overall heat transfer equation.

Slide 19 to 21

Q6. Explain coolant

Slide 22+23

Q7. Explain the combustion process inside engine.



Slide 25.

Q8. Sketch the strokes of engine.

Slide 28

Q9 Explain thermostat.

Slide 31 +32

Q10. Explain four phases of combustion.

Slide 33

Q11. Describe product of combustion.

Slide 34

Q12. Sketch engine ignition circuit.

Slide 40 to 43

Q13. Explain the followings

(a) Vane pump (b) Diaphragm pump

Slide 44 to 49

Q14. Sketch the followings

(a) Fuel filter (b) Injector

Slide 50

Q15. Explain nozzle

Slide 52

Q16. Copy the diagram on this slide.

Slide 56

Q17. How the engine is stopped?

Slide 57+58

Q18. Explain governor.

Slide 59.

Q19. Explain unit injector system.

Slide 60

Q20. Explain injector operation.

### **WEEK 7-EE 624 Process Control**

Study the notes in EE115+EE116 Folders & do the following exercises.

## **TUTORING LESSONS**

### **EE624**

### **EE116 Process Control System**

Lesson 1\_\_Lesson 2\_\_Lesson 3\_\_Lesson 4\_\_Lesson 5\_\_Lesson 6\_\_Lesson 7

Lesson 8\_\_Lesson 9\_\_Lesson 10

Password- iqytechnicalcollege


### **I006+ H012 Online Test**

Ref501

\_\_\_\_\_ provides the operation necessary to transform the sensor output into a form necessary to interface with other elements of process control loop.

|        |                              |   |                             |
|--------|------------------------------|---|-----------------------------|
| A      | Analogue signal conditioning | B | Digital signal conditioning |
| C      |                              | D |                             |
| Answer |                              |   |                             |

Ref504

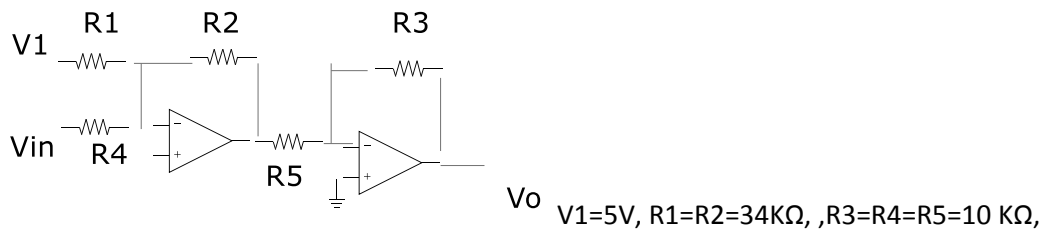

Vout for above circuit is

|        |                            |   |                            |
|--------|----------------------------|---|----------------------------|
| A      | $V_{out} = 1.7 V_{in} + 5$ | B | $V_{out} = 3.4 V_{in}$     |
| C      | $V_{out} = 1.7 V_{in}$     | D | $V_{out} = 3.4 V_{in} + 5$ |
| Answer |                            |   |                            |

Ref507

TTL 74LS 193 A CMOS 4035 ICs are used for

|        |                                     |   |                                   |
|--------|-------------------------------------|---|-----------------------------------|
| A      | Parallel in / Parallel out function | B | Serial in / Parallel out function |
| C      | Parallel in / Serial out function   | D | Serial in / Serial out function   |
| Answer |                                     |   |                                   |

Ref510

The number of data signal lines required for 7 segments display is

|        |   |   |    |
|--------|---|---|----|
| A      | 7 | B | 8  |
| C      | 9 | D | 10 |
| Answer |   |   |    |

Ref513

Events occur after the previous event is completed. The device is \_\_\_\_\_.

|        |                     |   |                    |
|--------|---------------------|---|--------------------|
| A      | Combinational logic | B | Sequential logic   |
| C      | Synchronous logic   | D | Asynchronous logic |
| Answer |                     |   |                    |

Ref516

$45_{10} =$

|        |            |   |            |
|--------|------------|---|------------|
| A      | $101101_2$ | B | $100101_2$ |
| C      | $111001_2$ | D | $101010_2$ |
| Answer |            |   |            |

Ref519

The device in which only one input at a time is activated to produce specific code at output is

|        |             |   |               |
|--------|-------------|---|---------------|
| A      | Decoder     | B | Encoder       |
| C      | Multiplexer | D | Demultiplexer |
| Answer |             |   |               |

Ref522

Latch can store

|        |                             |   |                              |
|--------|-----------------------------|---|------------------------------|
| A      | Only one bit of information | B | A number of bits at one time |
| C      |                             | D |                              |
| Answer |                             |   |                              |

Ref525

Decimal equivalence of 47H is

|        |    |   |     |
|--------|----|---|-----|
| A      | 71 | B | 781 |
| C      | 29 | D | 112 |
| Answer |    |   |     |

Ref528

Temperature is measured by a sensor with output  $0.02 \text{ V/}^\circ\text{C}$ . Determine ADC Reference & word size to measure 0 to  $100^\circ\text{C}$  resolution.

|        |              |   |              |
|--------|--------------|---|--------------|
| A      | 0.039V/ step | B | 0.078V/ step |
| C      | 0.156V/ step | D | 0.312V/ step |
| Answer |              |   |              |

Ref531

What is the HEX output of a bipolar 12 bit ADC with a 5 V reference for input  $-0.85\text{V}$

|        |     |   |      |
|--------|-----|---|------|
| A      | 54H | B | 108H |
| C      | 27H | D | 39H  |
| Answer |     |   |      |


Ref534

ADC has been developed to interface with microprocessor. Data from ADC is placed on \_\_\_\_\_. When appropriate command is issued.

|        |             |   |          |
|--------|-------------|---|----------|
| A      | Address bus | B | Data bus |
| C      | Control bus | D |          |
| Answer |             |   |          |

Ref537

The following is called \_\_\_\_\_.

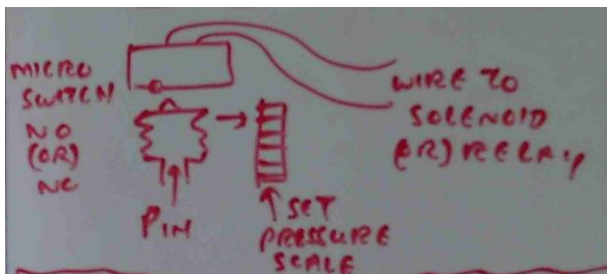

|   |                                      |   |                              |
|---|--------------------------------------|---|------------------------------|
| A | Bellow operated on-off controller    | B | On-off pressure control loop |
| C | Pneumatic force balance proportional | D |                              |

|  |            |  |  |
|--|------------|--|--|
|  | controller |  |  |
|  | Answer     |  |  |

Ref540

Derivative mode

|   |                                      |   |                    |
|---|--------------------------------------|---|--------------------|
| A | Stabilizes the process               | B | Resets the process |
| C | Compensates time lag in control loop | D |                    |
|   | Answer                               |   |                    |

## WEEK 18-ME 334 Airconditioning and Refrigeration

### TUTORING LESSONS

ME 334 Part 1

ME 334 Part 2

ME 334 Part 3

ME 334 Part 4

ME 334 Part 5

Study ME 334 part 1 & do the following exercises.

Listen to the audio explanation and diagram on the slides and answer the questions. You can write in English or Myanmar

Slide 1

Q1.Sketch & explain the function of condenser.

Slide 2

Q2.what is evaporator?

Slide 4 to 6

Q3. Sketch and explain the function of compressor.

Slide 8+9

Q4. Sketch the four strokes operation of compressor.

Slide 10 to 12

Q5. Sketch the complete refrigeration pipe line circuit of compressor, evaporator, condenser and explain the operation.

**Study ME 334 part 2 & do the following exercises.**

**Listen to the audio explanation and diagram on the slides and answer the questions. You can write in English or Myanmar**

Slide 18 to 20

Q6. Sketch the connection of pressure gauge and refrigerant container to charge the refrigerant into refrigeration system

**Study ME 334 part 3 & do the following exercises.**

**Listen to the audio explanation and diagram on the slides and answer the questions. You can write in English or Myanmar**

Slide 1 to 7

Q7. Explain refrigerant charging procedure with necessary sketches.

Slide 8

Q8. Sketch the diagram of thermostat and electrical circuit diagram of compressor motor.

Slide 9+10

Q9. Sketch the electrical circuit diagram for compressor motor power supply system.

Slide 13 to 15

Q10. Sketch electrical circuit diagram containing step down transformer, thermostat and compressor motor of refrigerator compressor motor power supply system.

Slide 16 to 20

Q11. explain the operation principle of compressor.

Study ME 334 part 4 & do the following exercises.

Listen to the audio explanation and diagram on the slides and answer the questions. You can write in English or Myanmar

Slide 1

Q12. Sketch the cross sectional view of compressor.

Slide 2

Q13. Sketch the refrigeration circuit connection of compressor, evaporator and condenser.

Slide 3 to 6

Q14. Explain the operation of TEV (Thermostatic expansion Valve or Refrigerant Control Valve with refrigerant control.

Slide 7.

Q15. Sketch installation diagram of refrigerator.

Slide 8

Q16. Sketch air ventilator and air duct.

Slide 9+10

Q17. How do you understand humidity?

Slide 12 to 14



Q18. What are the factors influencing comfort.

Slide 15

Q19. Sketch the arrangement of air distribution in a house.

Slide 16.

Q20. Sketch air duct installation diagram.

Slide 17+18

Q21. Sketch electrical circuit diagram of blower fan.

Slide 19+20

Q22. Sketch the various arrangements of air distribution ducts.

**Study ME 334 part 5 & do the following exercises.**

**Listen to the audio explanation and diagram on the slides and answer the questions. You can write in English or Myanmar**

Slide 1+2+4+5+8

Q23. Sketch the installation diagram of air ducts.

Slide 6+7

Q24. Provide four sketches of air diffusers.

Slide 9+10+12

Q25. Explain the split type air conditioner with necessary sketches.

Slide 11

Q26. Explain window type air conditioner with necessary sketch.

Slide 13+14

Q27. Explain air handler unit with refrigerant pipe.

Slide 16+17.

Q28. Sketch the complete refrigerant pipe line containing evaporator, compressor, condenser and explain the operation.

Slide 18+19

Q29. Sketch air distribution system for multistorey building

Q30. Sketch indoor and out door units of an air handler and label the components.

## TUTORING LESSONS

ME202 Part 1

ME202 Part 2

ME202 Part 3

Study ME202 Part 2 and do the following exercises.

Slide 1+2

Q13. Sketch the resultant force and moment acting on airfoil.

Slide 3

Q14. Sketch the graph of coefficient vs attack angle.

Slide 4

Q15. Sketch the rotation and distortion of fluid element.

Slide 5 to 7

Q16. Sketch

(a) Vortex sheet on camber line (b) Vortex sheet on chord line (c) Formation of wing vortex

Slide 8+9

Q17. Write the equation for inviscid compressible flow.

Slide 10

Q18. Write one dimensional flow equation.

Slide 11 to 14

Q19. Write the following equations

- (a) Inviscid momentum equation (b) Energy equation (c) Speed of sound (d) Stagnation pressure and stagnation density with stagnation temperature.

Slide 15 to 17

Q20.

A normal shock wave is formed in air where upstream Mach number is 2 and upstream temperature, pressure and density are 300 K, 1 atm (i.e., 1 atmospheric pressure, which is approximately  $1.01 \times 10^5 \text{ N/m}^2$ ) and  $1.2 \text{ kg/m}^3$  respectively. Calculate Mach number, velocity, static temperature, static pressure, stagnation temperature and stagnation pressure downstream of the shock. Assume  $\gamma = 1.4$ .

Slide 18 to 20

Q21. Write the equation for quasi one dimensional flow; nozzle and diffuser flow.

Slide 21

Q22. What the M values for the followings

- (a) Subsonic flow (b) Supersonic flow (c) Sonic flow.

## ME 202 Introduction to Aero Dynamics

Study ME202 Part 3 and do the following exercises.

Slide 1+2

Q23.

A supersonic flow at Mach number=2, temperature=300K, pressure=1atm and density= $1.2\text{kg/m}^3$  approaches a compression corner. An attached oblique shock with wave angle= $45^\circ$  is formed at the corner. Find the normal Mach numbers upstream and downstream of the shock. Also find  $M_2, p_2, p_{02}$ . Assume  $\gamma=1.4$ .

Slide 3

Q24. Explain the fundamental of viscous flow.

Slide 4 to 11

Q25. Write the equation for two dimensional poiseuille flow.

Slide 13.

Q26. Write the equation for density of liquid.

## ME 302 Automation-and-Robotics

### TUTORING LESSONS

ME 302 Part 1


ME 302 Part 2

ME 302 Part 3

Study ME 302 Part 1 and do the following exercises.

Slide 1 to 3

Explain the following layout.

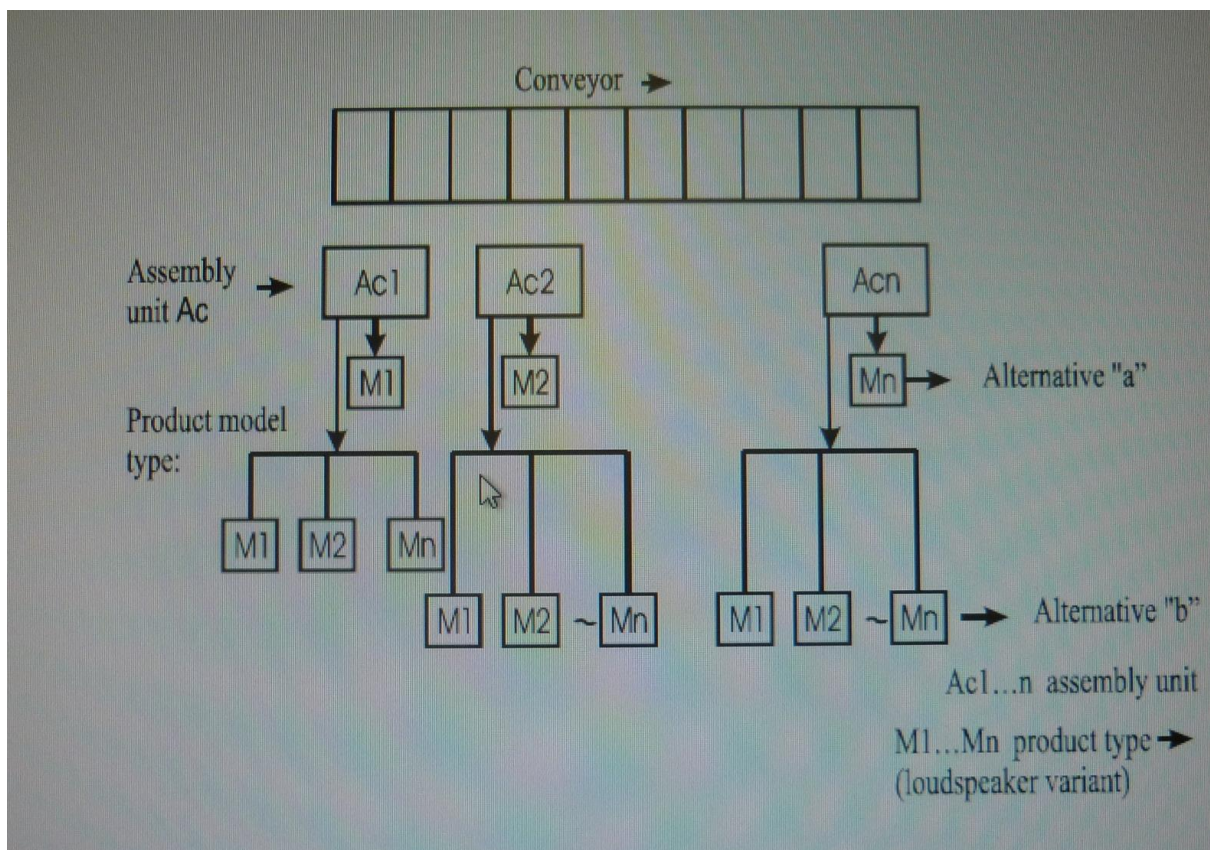

Slide 17

Q2. What kinds of operations can not be done by assembly machines.

### ME 302 Automation-and-Robotics Part 2

Slide 5

Q3. Provide an example of proposal for automation.

Slide 6

Q4. Explain end effector design.

Slide 7.

Q5. Explain robot arm grip design.

Slide 9+10

Q6. Explain feeding and storage of parts.

Slide 11

Q7. Describe feeder design.

Slide 18

Q8. Write the equation to calculate the volume of space occupied by single part.

Slide 19+20

Q9. What are the methods of re-filling.

### [ME 302 Automation-and-Robotics Part 3](#)

Slide 5

Q10. Describe assembly cell design.

Slide 11

Q11.

When  $N_{AC} = 22$ ,  $T_{2a} = 4[\text{sec}]$ ,  $N_M^{\text{max}} = 180000/\text{month}$

Calculate assembly line output.

### [ME 303 Computer Aided Design and Manufacturing \( Needs to do\)](#)

#### TUTORING LESSONS

ME303

### [Study folder ME 303 Computer Aided Design and Manufacturing](#)

[Page 9](#)

Q1. Describe the types of computer programs used in manufacturing.

Page 11

Q2. What are the production modules of pro-engineer.

Page 14

Q3.Explain ibm catia.

Page 17

Q4.What is Data CAD?

Page 21

Q5.What computer programs are used in design?

Page 27

Q6.Explain Cadtek system.

Page 29

Q7.Explain Design advisor.

Page 32

Q8.Explain Solid work.

Page 37

Q9.What factors are to be considered to select the CAD/CAM system?

Page 62

Q10.How will you create the new file in Pro-engineer?

Page 66

Q11.How will you define the co-ordinate system for machine tool?

Page 83

Q12.Explain the computer program using drilling holes with diameter 20mm.

Page 96

Q13.How will you define a co-ordinate system for machine tool?

Page 111

Q14.How will you calculate total machining time?

Page 127

Q15 Explain retrieve approach to optimize the machining sequence.

Page 139

Q16.Explain rapid pro-typing techniques.

Page 148

Q17.Explain laminated object manufacturing.

Page 150

Q18.Explain solid ground curing.

Page 157

Q19.Explain paper lamination technology.

Page 163

Q20.Explain design controlled automated fabrication.

Page 169

Q21.Explain

(a) Plastic (b) Metal

## Wk 14-ME 234 Wind Turbines

### TUTORING LESSONS

ME 234 Part 1

ME 234 Part 2

ME 234 Part 3

### Study ME 234 Part 1 & do the following exercises.

Slide 1+14

Q1.Sketch the wind turbine and label the components.

Slide 2

Q2.Write the factors to be concerned to sit the wind turbine.

Slide 4.

Q3. What are the planning constraints to install the wind turbines?

Slide 5

Q4. What are the separations between wind turbines?



Slide 6.

Q5 How the site is prepared before installing the wind turbine?

Slide 8 to 10

Q6. Describe the followings

(a) Conservation of mass (b) Conservation of energy (c) Conservation of momentum

Slide 11

Q7. Write the equation to calculate ideal wind power.

Slide 12+13

Q8. Explain wind energy theory.

Slide 15

Q9. What are the steps in planning the wind farm?

## **ME 201 Introduction to Fluid Mechanics ( Needs to do)**

### **TUTORING LESSONS**

ME201 Part 1

ME201 Part 2

ME201 Part 3\_

## **Wk 1- ME 201 Introduction to Fluid Mechanics Part 1**

Study the notes in ME201 Part 1 folder and do the following exercises.

Slide 1

Q1. Describe the nature of fluid.

Slide 2

Q2. Write continuum equation of fluid.

Slide 3

Q3.What are the properties of fluids

Q4. What is density?

Slide 5

Q5.What is viscosity?

Slide 6 to 8

Q6.Write the equation for viscosity.

Slide 9 to 11

Q7.Explain surface tension & write the equation.

Slide 12

Q8.What is compressibility?

Slide 13.

Q9. Outline the broad classification of fluid mechanic.

Slide 14.

Q10.Explain fluid statistics.

Slide 15 to 17

Q11.Write the equation for pressure.

Slide 18

Q12.Show pressure variation in the direction of gravity.

Slide 19

Q13.Define the followings.

(a) Pressure (b) Head

Slide 20

Q14.Explain measurement of pressure.

## Wk 3-ME 204 Engineering Fluid Mechanics

±

## ME 301 Fluid Dynamics ( Needs to do)

### TUTORING LESSONS

ME204

Study ME 301 folder & do the exercises

Slide 1

Q1. What kind of forces are acting on fluid particles?

Slide 2

Q2. Write the equation for compressible flow.

Slide 3

Q3. Express Navier Stokes equation and energy equation.

Slide 4

Q4. Write the equation for dissipation function.

Slide 5

Q5. Write the equation for incompressible flow.

Slide 6 to 8

Q6. Explain turbulent flow with diagram and express the graphs for instantaneous and average velocities.

Slide 9

Q7. Explain inviscid flow

Slide 10.

Q8.Explain boundary layer

ME 206 Introduction to Turbo Machinery ( Needs to do)

### TUTORING LESSONS

ME 206 Part 1

ME 206 Part 2

ME 206 Part 3

ME 206 Introduction to Turbo Machinery

Study the notes in ME 206 Part 1 Folder & do the following exercises.

Slide 1

Q1.Explain the basic mechanism of operating the turbine.

Slide 3

Q2.What are the components of turbine?

Slide 4 to 7

Q3.Sketch the simple turbine operation.

Slide 8

Q4.Explain meridional view of turbine.

Slide 11+12

Q5.Express the velocity triangle for aircraft landing.

Slide 13 to 16

Q6.Explain velocity triangles in turbo machinery.

Slide 17+18

Q7.Write the equations related to velocity triangles in turbo machinery.

Slide 20 to 22

Q8.Sketch the wind turbine & indicate the components.

Study the notes in ME 206 Part 2 Folder & do the following exercises.

Slide 1+2

Q9. Describe the forces acting on wind turbine blades.

Slide 3+4

Q10. Explain aerofoil operation and testing procedure.

Slide 5 to 8

Q11. A wind turbine is designed to work at a condition with a wind speed of 10 m/s and an air density of  $1.22 \text{ kg/m}^3$ . The turbine has blades with a NACA 0012 profile and is rotating at one revolution per second. The blade chord length is 0.5 m. Taking the design point at 85% maximum lift condition and ignoring the drag on the aerofoil, estimate the power output per unit blade span at a radius of 6 m for each blade.

Slide 11.

Q12. Describe wind turbine power control procedure.

Slide 12

Q13. Explain axial flow machine.

Slide 13 to 16

Q14. Explain radial and centrifugal flow machines.

Slide 17+18

Q15. Sketch velocity vector diagrams for stator and rotor of turbine.

Slide 19

Q16. Construct the cascade view of impeller.

Slide 20

Q17. Sketch the velocity diagram of impeller.

Slide 21 to 23

Q18. Write the equation for hydraulic turbine & explain its operation.

Study the notes in ME 206 Part 3 Folder & do the following exercises.

Slide 1

Q19. State the common design choice for constant axial velocity.

Slide 5+6

Q20.Explain the operation of turbo machines & system.

Slide 8

Q21.Sketch Enthalpy-Entropy diagram for turbine.

Slide 9+10

Q22.Explain dimensionless parameters for turbine machine.

Slide 11

Q23.Sketch the combined inlet & exit velocity diagrams of turbine.

Slide 12+13

Q24.Given a turbine blade row with constant axial velocity of 150 m/s at 5000 rpm on a mean radius of 0.7 m and an absolute flow angle at exit from the stator of 70 degree. The turbine operates with axial leaving flow and is a repeating stage. Calculate the flow coefficient , stage loading coefficient and reaction.

Slide 14

Q25. Write the equation to calculate the power coefficient of wind turbine.

Slide 15

Q26.Calculate the power output of the device at 10 rpm in a 10 m/s wind given that the turbine is 80 m in diameter and the density of air can be taken as  $1.15 \text{ kg/ m}^3$ .

Slide 16.

Q27.Write the equations to calculate the coefficients of hydraulic machines.

Slide 18

Q28. Write the equations to calculate the specific speed of hydraulic turbine.

Slide 19 to 21.

Q29.Explain pelton wheel turbine.

Slide 22

Q30.Explain analysis approach of pelton wheel turbine.

## **ME 205 Manufacturing Processes & Materials**

**Study ME 205 folder /CGVE 401 Folder 1 to 24 and do the following exercises.**

## TUTORING LESSONS

ME205 Part 1

ME205 Part 2

Slide 1

Q1. What are non conventional manufacturing processes?

Slide 2 to 5

Q2. Explain the followings.

- (a) Chemical machining
- (b) Electro-chemical machining
- (c) electro-chemical grinding
- (d) Electrical discharge machining
- (e) Wire electrical discharge machining
- (f) Laser beam machining
- (g) water jet machining
- (h) Abrasive jet machining

Slide 6+7

Q3. Explain (a) Process efficiency comparison (b) Tool wear (c) Personnel skills

Slide 8+9

Q4. What are significant factors causing tool wears?

Slide 10 to 12

Q5. Sketch conventional lathe knife & label the components.

Slide 13

Q6. Write Taylor's relation equation.

Slide 14

Q7. Write the formula to predict tool wear.

Slide 15

Q8. What are the factors that influence the useful life of tools.

Slide 17 to 22

Q9. Explain monitoring the condition of tools.

Slide 23+24

Q10. Explain acceptance sampling.

[ME 207 Chemical Thermodynamics](#)

## TUTORING LESSONS

ME207

Study ME 207 Folder & do the exercises

Slide 1

Q1. Sketch the graph for Molar Gibbs free energy.

Slide 2+4

Q2. Write the equation for Molar Gibbs free energy.

Slide 5+6

Q3. Write the equation for Liquid-liquid equilibrium.

Slide 7

Q4. Explain phase behaviour of solid liquid phase diagram.

Slide 8+9

Q5. What is the condition for equilibrium of chemical mixture?

Slide 10+11

Q6. Write the equation to calculate the difference in chemical potential of solid-liquid phase.

Slide 12

Q7. Sketch temperature VS mole fraction of ethanol.

Slide 13+14

Q8. Write the equation to calculate molar Gibbs free energy of the pure solid phase.

WEEK 17-ME 208 Hydrocarbons

## TUTORING LESSONS



ME208 Part 1

ME208 Part 2

Study ME208 Part 1 and do the following exercises.

Slide 3

Q1.Explain Benzene.

Slide 6+78

Q2.What are the viscosities of (a) Ethanol (b) Acetone (c) Toluene(d) n-hexane?

Slide 9+10

Q3.What are the acoustic impedance of Acetone ,Ethanol ,Glycerol?

Slide 11

Q4.What are thermal conductivities of Acetone, Methanol, Benzene?

Slide 12

Q5.Explain electrical properties of hydro-carbons.

Slide 13+14

Q6.Explain optical properties of hydro-carbons.

Slide 15+16

Q6.Explain physical properties of crude oil.

Slide 17 to 19

Q7.Show one example for each of light crude oil, medium crude oil and heavy crude oil and describe their properties.

Slide 20.

Q8.Explain viscosity of blended crude oil.

Slide 21

Q9.Write the equation for coefficient of thermal expansion of crude oil.

Study ME208 Part 2 and do the following exercises.

Slide 1+2

Q10.Explain the followings

- (a) Thermal conductivity (b) Viscosities of blends of crude oil

Slide 4

Q11.What are the properties of Gasoline-ethanol blends.

Slide 5

Q12.Explain refinement to RVP.

Slide 6

Q13.What is thermal conductivity of petroleum?

Slide 7 to 9

Q14.Explain the following physical properties of kerosene

- (a) Density (b) Solid deposition (c)Viscosity

Slide 12

Q15.Write note on diesel fuel.

Slide 13 to 15

Q16.Explain the followings for diesel fuel.

- (a) Refractive index (b) Electrical conductivity (c) Lubricity

Slide 16

Q17.What are density and viscosity of residual oil.

Slide 17

Q18.Explain (a) Solid deposition from heavy fuel oil (b) Vapour pressure of residual fuel oil.

Slide 19 to 23

Q19.Explain the followings.

- (a) Methanol (b) Ethanol (c) Methanol -gasoline blend (d) Ethanol-gasoline blend

Slide 24 to 26

Q20.Explain bio-diesel fuel.

Q21.What are viscosity and particulate deposition of bio-diesel fuel?

## WEEK 16-ME 634 Pneumatics

### TUTORING LESSONS

ME634 Part 1

ME634 Part 2

ME634 Part 3

ME634 Part 4

Study ME 634 Pneumatics part 1 and do the following exercises.

Slide 1

Q1.Explain transmission of force by fluid.

Slide 2

Q2.Write the equation to calculate pressure.

Slide 4

Q3.Sketch the effective area of piston.

Slide 5

Q4.Explain flow and pressure drop.

Slide 6.

Q5.What are the natures of the pressure at upstream and downstream.

Slide 7

Q6.Explain flow through orifice to atmosphere.

Slide 8+9

Q7.Explain the followings

- (a) Atmospheric pressure (b) Vacuum pressure (c) Gauge pressure versus absolute pressure.

Slide 10

Q8.Explain the pressure in liquid.

Slide 12

Q9.An air receiver with a volume of  $6 \text{ m}^3$  must be filled with compressed air to a maximum pressure of 900 kpa ( 9 bar ) . Calculate the volume of free air (FA) to be pumped by the compressor.

Slide 13

Q10.Explain Charles law

Slide 14+15

Q11.Explain Gay Lussac's law

Q12.Explain the concept of power transmission.

Slide 16

Q13.Explain the relationship of force, velocity, pressure and flow rate.

Slide 17.

Q14 Sketch the basic pneumatic system by applying block diagram and pneumatic symbols.

Slide 18 to 20

Q15.Sketch the following positions of valves.

- (a) Actuated position (b) Non actuated position (c) Centre position.

[ME 634 Pneumatics](#)

**Study ME 634 Pneumatics part 2 and do the following exercises.**

Slide 1+2

Q16.Explain the uses of two ports, three ports, four ports and five ports valves.

Slide 3

Q17. Sketch the mechanism of rotary plug valve.

Slide 4 to 8

Q18. Explain the followings.

- (a) Normally closed and normally open valves
- (b) Methods of valve actuation
- (c) Spring actuated valves

Slide 9

Q19. Sketch the followings.

- (a) Pedal
- (b) plunger
- (c) Spring
- (d) Detent
- (e) Solenoid valve
- (f) Spring centred

Slide 10 to 13

Q20. Explain spool valve, flat slide valve and poppet valve.

Slide 14

Q21. Describe spool-poppet valve with sketch.

Slide 15 to 17

Q22. Explain toggle disc valve.

Slide 18 to 20

Q23. Explain the followings

- (a) Cross over condition
- (b) Special condition
- (c) Valve conversion.

## ME 634 Pneumatics

Study ME 634 Pneumatics part 3 and do the following exercises.

Slide 1+2+3

Q24. Sketch positive overlap and negative overlap.

Slide 4 to 7

Q25. Sketch Normally closed and Normally open valve

Q26. Explain actuator control.

Slide 8+9

Q27.Explain time delay valve.

Slide 12+13

Q28.Explain the followings

(a)Variable restrictor with free reverse flow (b) Cam roller operated flow control

Slide 14+15

Q29.Explain quick exhaust speed control.

Slide 16+17

Q30.Explain power valve exhaust port speed control.

Slide 18+19

Q31.Explain air motors.

[ME 634 Pneumatics](#)

[Study ME 634 Pneumatics part 4 and do the following exercises.](#)

Slide 1+2

Q32.Describe pneumatics sensors.

Slide 3 to 5

Q33. Describe back pressure sensor for contact sensing.

Slide 6+7

Q34.What is proximity sensor?

Slide 8+9

Q35.Sketch sensor circuit.

Slide 10

Q36.Explain pneumatics governor.

**WK 2-ME 203 Control Engineering**

## TUTORING LESSONS

ME 203 Part 1

ME 203 Part 2

ME 203 Part 3\_

Study ME 203 Part 1 and do the following exercises.

Slide 1

Q1. Sketch basic feedback control structure.

Slide 2

Q2. Write the differential equations for control function.

Slide 3

Q3. Write the equation for Laplace transform.

Slide 5+6+8+9

Q4. Write an example equation for state-space representation.

Slide 7

Q5. Sketch simple RC circuit.

Slide 11

Q6. Write state and output equation.

Slide 12+13

Q7. Write MATLAB entry for

$$G(S) = (2S+1) / (S^2+4S+3)$$

Slide 14 to 18

Q8. Express interconnecting models in MATLAB for the followings.

(a)  $G = G1 * G2$  (b)  $G = G1 + G2$

Slide 19

Q9. Write single pole transfer function equation

[WEEK 14- ME 534 Numerical Control Part 1](#)

### TUTORING LESSONS

ME534 Part 1

ME534 Part 2

ME534 Part 3

ME534 Part 4

ME534 Part 5

ME534 Part 6

ME534 Part 7

**Study Numerical Control Part 1 & do the following exercises.**

Slide 1

Q1. What are technical limitations of numerical control machines?

Slide 2

Q2. Describe the breakdown time spent by average workshop in machine shop.



Slide 3

Q3. Sketch the flow diagram of numerical control process.

Slide 5+6

Q4. Sketch the machine control unit & work table arrangement.

Slide 7 to 9

Q5. Sketch the work processing system of two axis machine.

Slide 10 to 12

Q6. Sketch closed loop control system.

Slide 13 to 20

Q7. Explain the followings

Contouring (b) Cartesian co-ordinate (c) Two axis tape control (d) Four or five axis tape control

## ME 534 Numerical Control Part 2

Study Numerical Control Part 2 & do the following exercises.

Slide 1

Q8. Explain incremental system.

Slide 2+3+4

Q9. Explain absolute system.

Slide 5 to 7

Q10. Explain zero shift system.

Slide 8

Q11. Explain binary coded decimal system.

Slide 9+10

Q12. What is ASCII code.

Slide 11+12

Q13. What is sequence number?

Slide 14

Q14. Explain the followings

- (a) Rapid (b) Feed

Slide 15 to 18

Q15. Explain the followings.

- (a) Drill cycle (b) Dwell cycle (c) Cancel cycle

### ME 534 Numerical Control Part 3

Study Numerical Control Part 3 & do the following exercises.

Slide 1 to 3

Q16. Explain

- (a) Feed rate (b) Spindle speed (c) Depth selection


Slide 4 to 5

Q17. Explain the followings.

- (a) M00 (b) M01 (c) M02 (d) M06

Slide 7 to 14

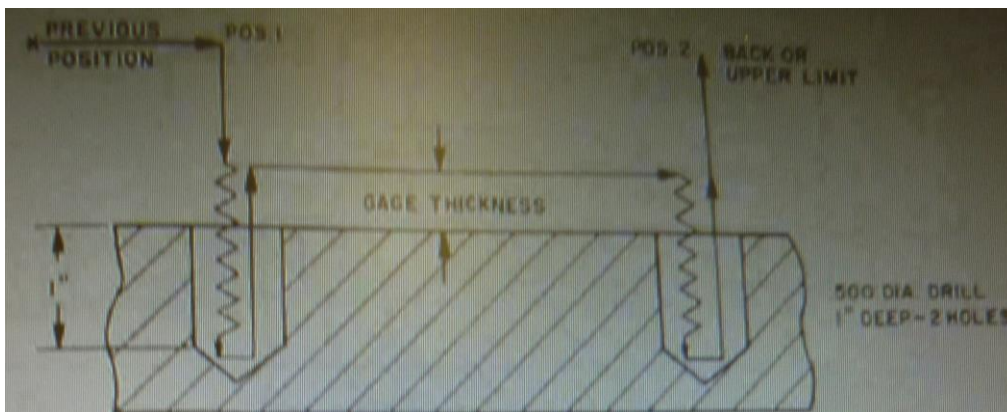Q18. Write the CNC Program for the following operation.



For (a) Drill Programming (b) Dwell programming (c) Bore programming (d) Tap Programming

Slide 15 to 18

Q19. Explain the followings

- (a) O001 (b) N002 (c) N003 (d) N004 (e) O005

## ME 534 Numerical Control Part 4

Study Numerical Control Part 4 & do the following exercises.

Slide 1 to 5

Q20.Explain the followings.

(a) O007 (b) N008 (c) O009 (d) N010 (e)O011 (f) N012 (g) N013 (h)N014 (i) N015

Slide 6 to 10

Q21.Explain linear interpolation and circular interpolation.

Slide 11 to 15

Q22.Explain the CNC program for linear interpolation and circular interpolation.

Slide 16+17

Q23.Write the equation to calculate Z depth & sketch the diagram.

Slide 18 to 20

Q24.Explain tool length compensation.

## ME 534 Numerical Control Part 5

Study Numerical Control Part 5 & do the following exercises.

Slide 1 to 4

Q25.Sketch CNC lathe and label the components.

Slide 5+6

Q26.Write spindle speed format.

Slide 7 to 10

Q27.What functions are done with the followings?

(a) G (b) X/X (c) I/K (d) A (e)F (f)V (g)S (h) T (i) C (j) D ( K) M

Slide 12 to 16

Q28.Explain the following operation.

N420 G02 X23188 Z20000 I23188 K 29688

Slide 20

Q29.Explain threading operation.

## TUTORING LESSONS

ME434 Part 1

ME434 Part 2

ME434 Part 3

Study ME434 Part 1 and do the following exercises.

Slide 1

Q1.List the performance characteristics of robotics.

Slide 2 to 9

Q2.Describe the methods used for measuring robot accuracy.

Slide 10

Q3.Explain transmission of energy with sketch.

Slide 11+12

Q4.Write the formula to calculate the power of manipulator.

Slide 15+16

Q5.Describe interfacing link.

Slide 17 to 20

Q6.Sketch the followings

- (a) Transmitter circuit
- (b) Signal output condition
- (c) Connection of input connection to controller

Study ME434 Part 2 and do the following exercises.

Slide 1 to 5

Q7.Sketch remote operator's station for controlling two robotic work cells.

Slide 7

Q8.Sketch dual gripper.

Slide 8

Q9. Sketch safety joint and alarm switch for an end effector.

Slide 11

Q10. Sketch inside diameter gripper.

Slide 13

Q11. Sketch vacuum gripper.

Slide 14

Q12. Sketch dual magnetic gripper.

Slide 15 to 20

Q13. Explain the followings.

- (a) Contact sensor
- (b) Proximity sensor
- (c) Vision system as non contact sensor
- (d) Limit switch
- (e) Thermocouple sensor.

**Study ME434 Part 3 and do the following exercises.**

Slide 1+2

Q14. Explain robotic work transfer with sketch.

Slide 3

Q15. Sketch machine transfer work cell.

Slide 6 to 9

Q16. Sketch the circuit consisting of left & right motor

## **EE 617 Building Electrical and Mechanical System Part 1**

Study the notes in EE307 (EE617) Folder & Submit the solar energy design project

### EE307 Energy Efficient Building Design

#### TUTORING LESSONS

[EE307 Part 1](#)   [EE307 Part 2](#)   [EE307 Part 3](#)   [EE307 Part 4](#)

[EE307 Part 5](#)   [EE307 Part 6](#)

## Test & Assessment

[http://www.filefactory.com/file/5laxij9trib1/n/K041\\_Test\\_pdf](http://www.filefactory.com/file/5laxij9trib1/n/K041_Test_pdf)

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

Password- [iqytechnicalcollege](#)

ME 104 Machine Principle ( 2 pt) ( Needs to do)

### **ME104**

### TUTORING LESSONS

#### EE105 Electrical Installation Design

#### EE107 Electrical Equipments

[Lesson 1](#) [Lesson 2](#) [Lesson 3](#) [Lesson 4](#)

#### EE105 Electrical Installation Design

#### EE107 Electrical Equipments

Study the powerpoints in

EE105+107 Power Point Part 1

EE105+107 Power Point Part 2

EE105+107 Power Point Part 3

EE105+107 Power Point Part 4

and do the following exercises.

#### EE105+107 Power Point Part 1

Q1. Describe the structure of wiring rules

Q2. Take the practice on problem in presentation 48.

### **EE105+107 Power Point Part 2**

Q3. Determine the maximum route length of 6 mm<sup>2</sup> bare copper single phase consumer main with maximum demand of 80A and permissible voltage drop of 4.3 V.

### **EE105+107 Power Point Part 3**

Q4.

Calculate the voltage drop in each segment of a 3 phase 400 volt non-domestic installation consisting of the followings.

#### Consumer main

Phase = 3      Maximum demand 45 Amp      Route length = 25 m

Cable size 16 mm<sup>2</sup>

Cable configuration V90 Single core thermo plastic and sheathed copper conductor

#### Cable installation

The circuit is enclosed in heavy duty rigid thermoplastic conduit with no other circuits. Conduit is buried in the ground having an ambient soil temperature of 25 °C and has a top cover of 0.65 m.

#### Sub main

Phase = 3 Maximum demand = 35 A, Route length = 35 m

Cable size = 10 mm<sup>2</sup>

#### Cable configuration

V90 Single core thermoplastic and sheathed copper conductors structure in trefoil formation and installed in single circuit configuration unenclosed in air

#### Final sub circuit

Phase = 1 Maximum demand = 20 Amp      Route length = 35 m

Cable size = 4 mm<sup>2</sup>

Cable configuration - V90 two cores and earthed thermoplastic and sheathed copper conductors

Cable installation - The cables are clipped to the building structure and installed in single circuit configuration , unenclosed in air.

Does this portion of the installation comply with the voltage drop requirement of AS/NZS 3000 ?

### **EE105+107 Power Point Part 4**

Q5.

A final sub-circuit supplies a load consisting of a range in a domestic installation and is protected by 32A Type C circuit breaker. Determine the maximum internal fault loop impedance of final sub circuit based on 230V when supply is unavailable.

## EE106 Advanced Electrical Wiring

+

## EE108 Electrical Fault Finding

### TUTORING LESSONS

[Lesson 1](#) [Lesson 2](#) [Lesson 3](#) [Lesson 4](#)

### Test & Assessment

<http://www.classroomclipboard.com/503511/Home/Test/334df2651a9440aa8fe25532f0e3d7c5#/InitializeTest.xaml>

Type your name Put the following access code

NY78T

Study the notes

Then do the following exercises.

1) Ref 604

A final subcircuit supplies a load consisting of 25A outlet and protected by 25A HRC fuse. Determine the maximum fault loop impedance of final subcircuit & based on 230V.

2) Ref 603

Final subcircuit supplies a load consisting of a range in domestic installation & is protected by 32A CB . Determine maximum internal fault loop impedance of final subcircuit based on 230V.



3) Ref 602

Write the formula to calculate the voltage drop in electrical cable

4) Ref 601

Describe the overview of AS 3000 Electrical wiring rule.

5) Ref 600

What are the requirements to install the switch board?

6) Ref 599

Explain the installation of switch board

7) Ref 598

Explain the operation principle of RCD with sketch

8) Ref 597

Explain the requirements of switch board in domestic electrical installation

9) Ref 596

Sketch the connection of a typical switch board

10) Ref 595

Describe the followings

(a) Basic protection principle (b) Overload and short circuit protection

11) Ref 594

Explain the explosion protection techniques.

12) Ref 593

Sketch TPS wiring system

13) Ref 592

Explain underground wiring system with sketch

14) Ref 591

Explain the following equipments

(a) Water heater (b) Cooking appliances (c) Motor

15) Ref 590

Sketch earthing system and earthing arrangement

16) Ref 589

Explain electrical installation safety testing procedures

17) Ref 588

Sketch the polarity testing circuits

18) Ref 587

What are the types of RCD?

19) Ref 586

Outline the overload protection devices

20) Ref 585

(a) Explain earthing protection

## [EE116 Process Control System](#)

### [EE115 Basic Analogue & Digital Electronics](#)

## [EE116 Process Control System](#)

### [TUTORING LESSONS](#)

[Lesson 1](#) [Lesson 2](#) [Lesson 3](#) [Lesson 4](#) [Lesson 5](#) [Lesson 6](#) [Lesson 7](#)

[Lesson 8](#) [Lesson 9](#) [Lesson 10](#)

### [Test & Assessment](#)

[http://www.filefactory.com/file/46zzpcym7uqz/n/l006\\_H012\\_Online\\_Test\\_1\\_Question.pdf](http://www.filefactory.com/file/46zzpcym7uqz/n/l006_H012_Online_Test_1_Question.pdf)

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

Password- **iqytechnicalcollege**

### Study the followings

EE115+EE116 Files

And do the following exercises.


#### I006+ H012 Online Test

Ref501

\_\_\_\_\_ provides the operation necessary to transform the sensor output into a form necessary to interface with other elements of process control lop.

|               |                              |   |                             |
|---------------|------------------------------|---|-----------------------------|
| A             | Analogue signal conditioning | B | Digital signal conditioning |
| C             |                              | D |                             |
| <b>Answer</b> |                              |   |                             |

Ref504

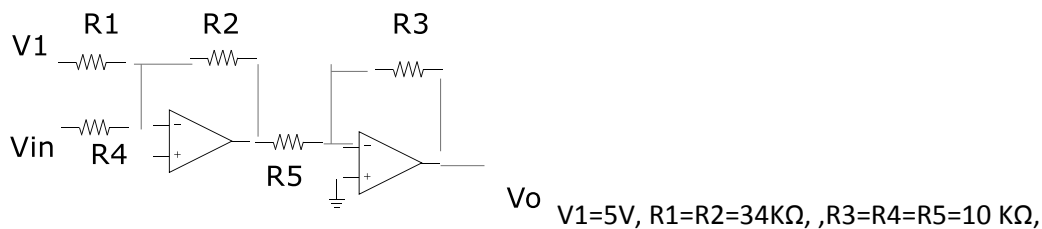

Vout for above circuit is

|   |                            |   |                            |
|---|----------------------------|---|----------------------------|
| A | $V_{out} = 1.7 V_{in} + 5$ | B | $V_{out} = 3.4 V_{in}$     |
| C | $V_{out} = 1.7 V_{in}$     | D | $V_{out} = 3.4 V_{in} + 5$ |

|        |  |
|--------|--|
| Answer |  |
|--------|--|

Ref507

TTL 74LS 193 A CMOS 4035 ICs are used for

|        |                                     |   |                                   |
|--------|-------------------------------------|---|-----------------------------------|
| A      | Parallel in / Parallel out function | B | Serial in / Parallel out function |
| C      | Parallel in / Serial out function   | D | Serial in / Serial out function   |
| Answer |                                     |   |                                   |

Ref510

The number of data signal lines required for 7 segments display is

|        |   |   |    |
|--------|---|---|----|
| A      | 7 | B | 8  |
| C      | 9 | D | 10 |
| Answer |   |   |    |

Ref513

Events occur after the previous event is completed. The device is\_\_\_\_\_.

|        |                     |   |                    |
|--------|---------------------|---|--------------------|
| A      | Combinational logic | B | Sequential logic   |
| C      | Synchronous logic   | D | Asynchronous logic |
| Answer |                     |   |                    |

Ref516

$45_{10} =$

|        |            |   |            |
|--------|------------|---|------------|
| A      | $101101_2$ | B | $100101_2$ |
| C      | $111001_2$ | D | $101010_2$ |
| Answer |            |   |            |

Ref519

The device in which only one input at a time is activated to produce specific code at output is

|        |             |   |               |
|--------|-------------|---|---------------|
| A      | Decoder     | B | Encoder       |
| C      | Multiplexer | D | Demultiplexer |
| Answer |             |   |               |

Ref522

Latch can store

|        |                             |   |                              |
|--------|-----------------------------|---|------------------------------|
| A      | Only one bit of information | B | A number of bits at one time |
| C      |                             | D |                              |
| Answer |                             |   |                              |

Ref525

Decimal equivalence of 47H is

|        |    |   |     |
|--------|----|---|-----|
| A      | 71 | B | 781 |
| C      | 29 | D | 112 |
| Answer |    |   |     |

Ref528

Temperature is measured by a sensor with output  $0.02 \text{ V} / ^\circ \text{C}$ . Determine ADC Reference & word size to measure 0 to  $100^\circ \text{C}$  resolution.

|        |              |   |              |
|--------|--------------|---|--------------|
| A      | 0.039V/ step | B | 0.078V/ step |
| C      | 0.156V/ step | D | 0.312V/ step |
| Answer |              |   |              |

Ref531

What is the HEX output of a bipolar 12 bit ADC with a 5 V reference for input -0.85V

|        |     |   |      |
|--------|-----|---|------|
| A      | 54H | B | 108H |
| C      | 27H | D | 39H  |
| Answer |     |   |      |


Ref534

ADC has been developed to interface with microprocessor. Data from ADC is placed on \_\_\_\_\_.  
When appropriate command is issued.

|        |             |   |          |
|--------|-------------|---|----------|
| A      | Address bus | B | Data bus |
| C      | Control bus | D |          |
| Answer |             |   |          |

Ref537

The following is called \_\_\_\_\_.

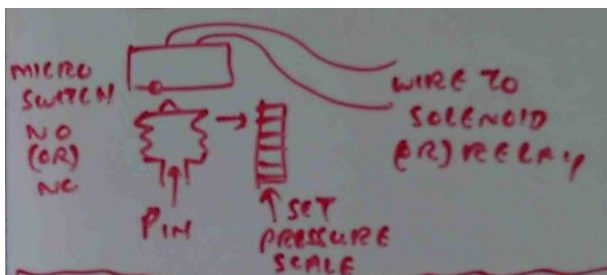

|        |   |   |                              |
|--------|---|---|------------------------------|
| A      | Bellow operated on-off controller               | B | On-off pressure control loop |
| C      | Pnuematic force balance proportional controller | D |                              |
| Answer |   |   |                              |

Ref540

Derivative mode

|               |                                      |   |                    |
|---------------|--------------------------------------|---|--------------------|
| A             | Stabilizes the process               | B | Resets the process |
| C             | Compensates time lag in control loop | D |                    |
| <b>Answer</b> |                                      |   |                    |

## WK 5- EE117 Solar Electrical System

### EE117 Solar Electrical System

#### TUTORING LESSONS

[Lesson 1](#) [Lesson 2](#) [Lesson 3](#) [Lesson 4](#) [Lesson 5](#) [Lesson 6](#)

Password- [iqytechnicalcollege](#)

#### Test & Assessment

Read the following notes

[K025\\_Note\\_1](#)

[K025\\_Note\\_2](#)

And then

[K025\\_Tutorials.zip](#)

Study the followings EE117 Lessons

Then do the following exercises

Q1.Explain the operation principle of PV cell



Q2. Sketch the interconnection of PV modules

Q3. Write the equation for PV power conversion.

Q4. Find the output of a module operating at maximum power point giving the followings

Typical maximum power at STC = 77w, NOCT = 49 deg C Power output coefficient  $\gamma = -0.38\%$  Ambient temperature = 35 Deg C  
Irradiance = 865 w/ m<sup>2</sup>

Q5. Describe the production procedure of standard silicon solar cell.

Q6. Calculate daily energy output of 77W. Lead acid battery charging ambient temperature  $f_{derate} = 1$ ,  $V_{module} = 14V$ , Irradiation = 4 wh / m<sup>2</sup>, maximum module power rating = 72 W, NOCT = 49 deg C.

Q7. Calculate the daily energy output of a 100W poly crystalline module operating under the following conditions.

Maximum power point tracking regulator MPPT, Ambient day time temperature 25 Deg C, Irradiation 5.5 KWH / m<sup>2</sup>. Environment with annual maintenance only. The manufacturer who tests the modules to international standard guarantees the maximum modules power rating to be 95W and NOCT = 49 Deg C.  $\gamma = 0.5\%$

Q8. Describe solar radiation and shading assessment.

Q9. Write the equation for manual calculation of irradiation data.

Q10. Sketch the followings (a) Series PV system (b) Parallel PV system (c) PV lighting system

Q11. Sketch PV water pumping system.

## EE119 Electrical Risk Assessment

## EE120 Electrical Contracting

### EE119 Electrical Risk Assessment

#### TUTORING LESSONS

##### Lesson 1

##### Test & Assessment

<http://www.classroomclipboard.com/503511/Home/Test/eafdcf3b16cf46908aad44c6d604b550#/InitializeTest.xaml>

Type your name Put the following access code

P2PLK

Password- **iqytechnicalcollege**

Study WOC Mgt 104-E071 Lessons & then do the following exercises

2) Ref 584

Explain the features of maintenance and specialist work

3) Ref 583

Explain purchasing procedures in electrical contracting

4) Ref 582

Explain pre-job planning in electrical contracting.

5) Ref 581

Brifely explain the specification for installing the high voltage cable.

6) Ref 580

What are the factors to be considered by electrical contractor before establishing the business?

7) Ref 579

Describe the job accounting system in electrical contracting

8) Ref 578

Explain the required paper works in electrical contracting

9) Ref 577

Explain insurance in electrical contracting

10) Ref 576

Explain contract bid work

Ask for study note & assignment by e-mail

ME 109 Engineering Drawing ( Needs to do)

EE301 Advanced Electrical Drafting ( Needs to do)

## EE301 Advanced Electrical Drafting

### TUTORING LESSONS

Stage 1 Part 3.zip

[http://www.filefactory.com/file/c0cb8f5/n/Stage\\_1\\_Part\\_3.zip](http://www.filefactory.com/file/c0cb8f5/n/Stage_1_Part_3.zip)

Stage 1 Part 4.zip

[http://www.filefactory.com/file/c0cc1cd/n/Stage\\_1\\_Part\\_4.zip](http://www.filefactory.com/file/c0cc1cd/n/Stage_1_Part_4.zip)

**Password---** joe2013

### **1WiringInstallationDrawing**

### **7MachineDriveSystems**

### **8PowerElectronicsDevices**

Stage 4 Part 11.zip

[http://www.filefactory.com/file/c0cc540/n/Stage\\_4\\_Part\\_11.zip](http://www.filefactory.com/file/c0cc540/n/Stage_4_Part_11.zip)

**Password---** joe2013

### **AutoCAD\_2D\_3D\_Lessons**

**Stage 4 Part 1A.zip**

[http://www.filefactory.com/file/c0cc226/n/Stage\\_4\\_Part\\_1A.zip](http://www.filefactory.com/file/c0cc226/n/Stage_4_Part_1A.zip)

**Stage 4 Part 12.zip**

[http://www.filefactory.com/file/c0cc566/n/Stage\\_4\\_Part\\_12.zip](http://www.filefactory.com/file/c0cc566/n/Stage_4_Part_12.zip)

Password--- joe2013

Symbol A

Symbol B

Symbol C

Symbol D

Symbol E

Symbol F

Symbol G

Stage 4 Part 22.zip

[http://www.filefactory.com/file/c0cc83e/n/Stage\\_4\\_Part\\_22.zip](http://www.filefactory.com/file/c0cc83e/n/Stage_4_Part_22.zip)

Password--- joe2013

Assessment-In class assessment

E071\_MEM09004\_Tutorial

E071\_MEM09004\_Tutorial\_Mod.zip

Stage 4 Part 14.zip

[http://www.filefactory.com/file/c0cc684/n/Stage\\_4\\_Part\\_14.zip](http://www.filefactory.com/file/c0cc684/n/Stage_4_Part_14.zip)

Password--- joe2013

Submit the drawing tutorial assignment



---

**Week 1**-Unit Code: EE301

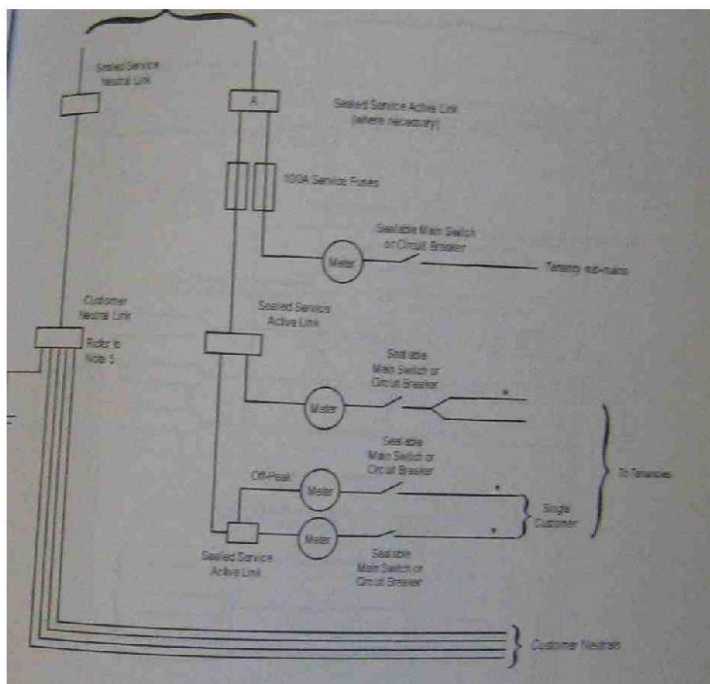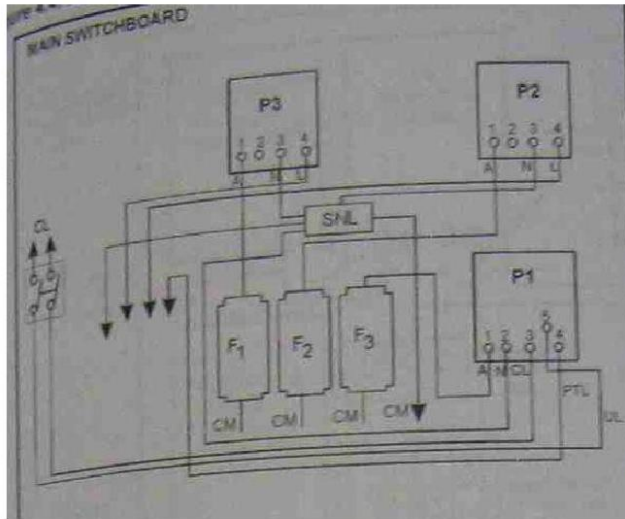
# **Advanced Electrical Drafting**

Do the electrical drawing exercises in attached folder

(Do not copy the given diagram, it is just a reference, you need to draw your own sketch by computer)



(3) Sketch the given circuit

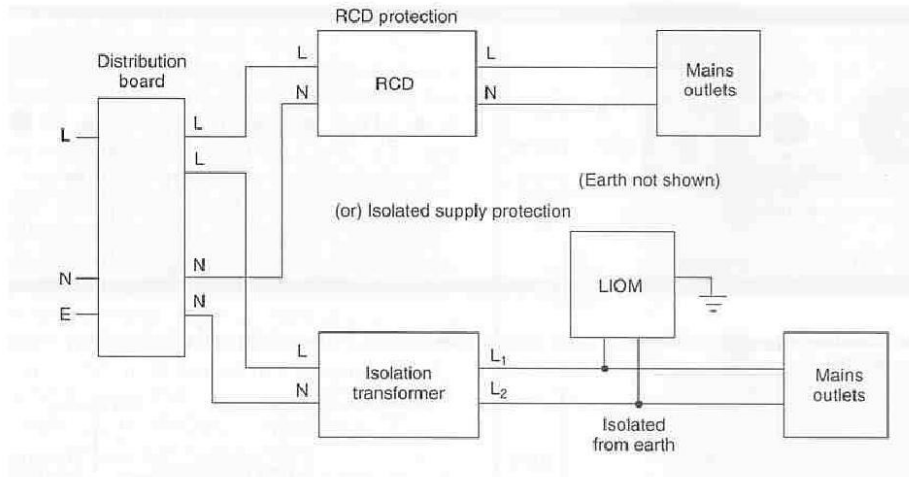

(4)


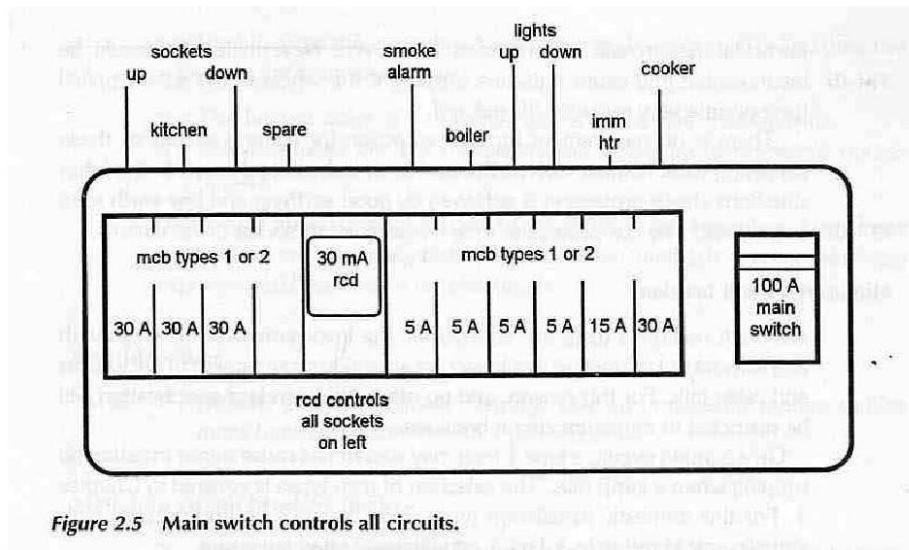


Figure 2.5 Main switch controls all circuits.

(5)

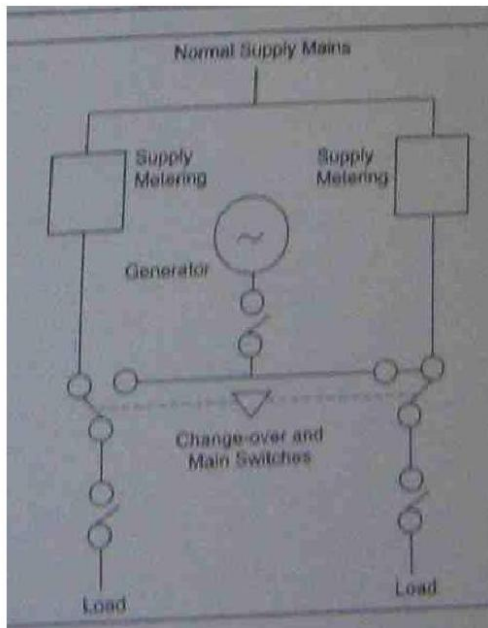




Reference: Specification (1)

(1) Write the important aspects of the specifications for electro medical equipments

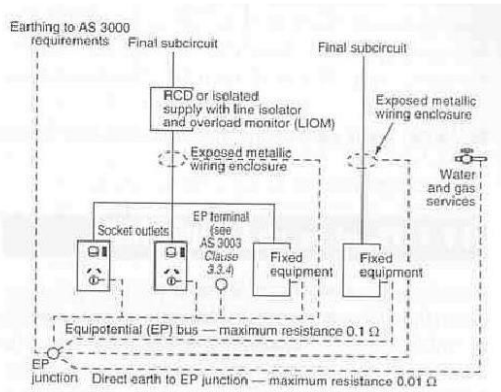(2) Draw the following circuits by computer





**(2)Reference: Service Rule 3****Job (3)**


You need to install a stand by generating plan for a small factory.

Prepare the specifications and design diagram for the following aspects

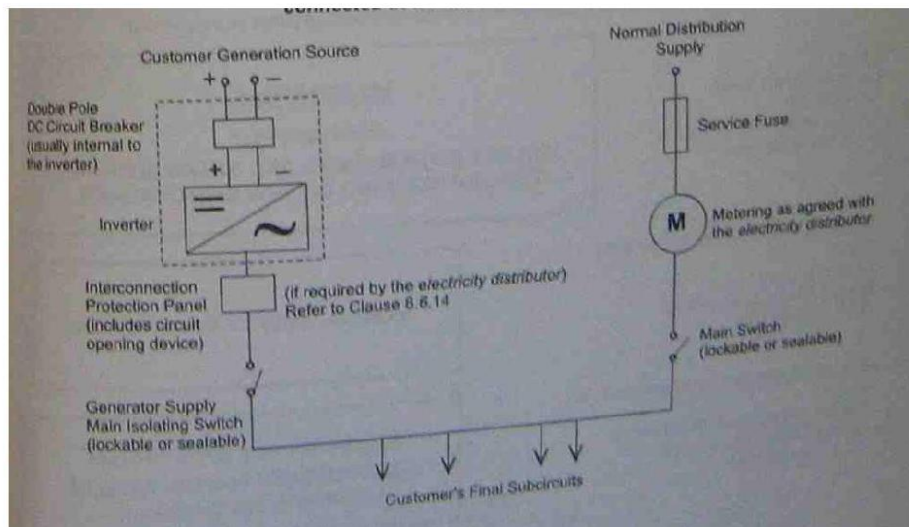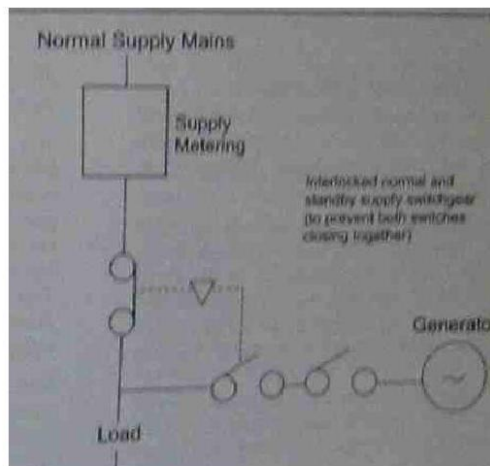
(1)Condition of use, (2)spacing for conductors, (3)change over equipments, (4)Operating procedure, (5)protection

Reference Diagram (Do not copy the given diagram, it is just a reference, you need to draw your own sketch by computer)




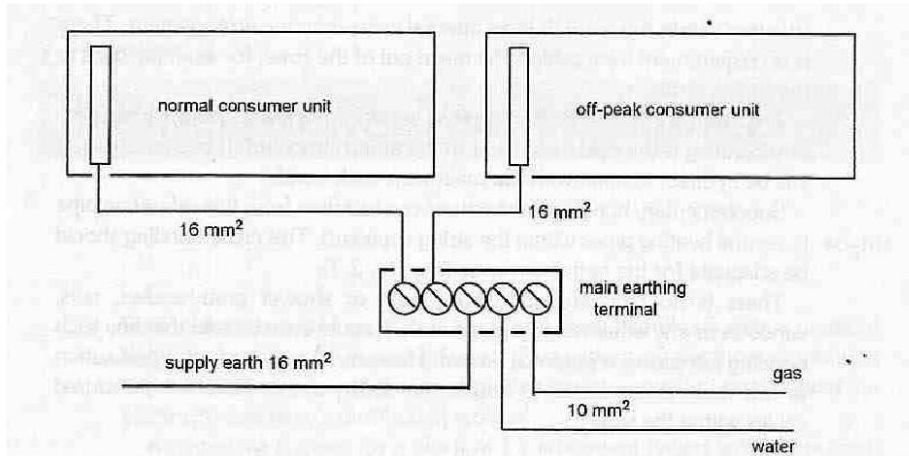


(6)

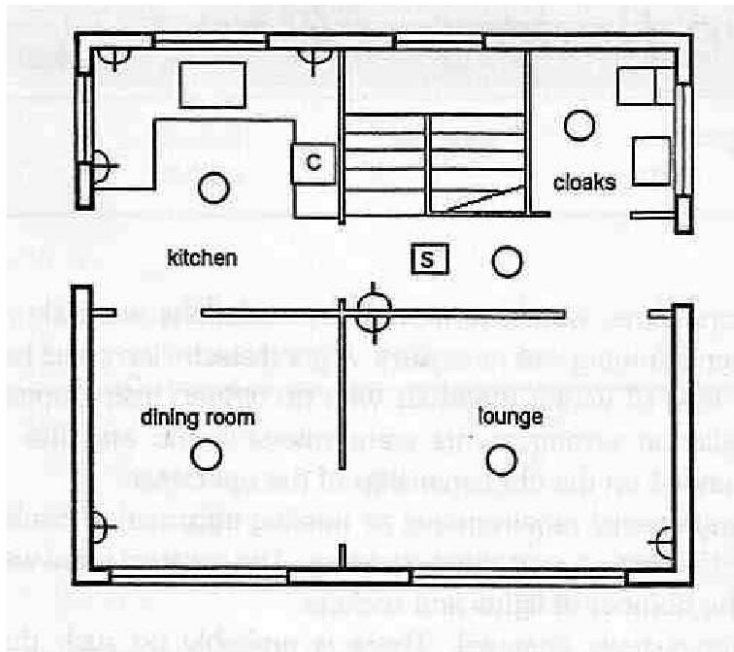


(7)

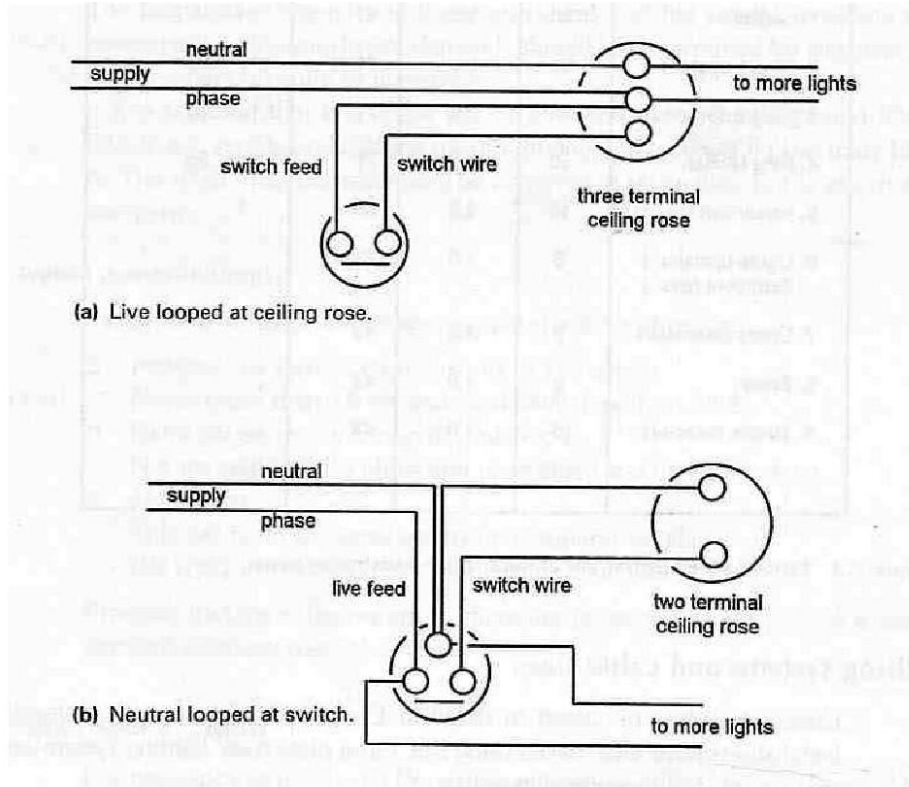


(8)

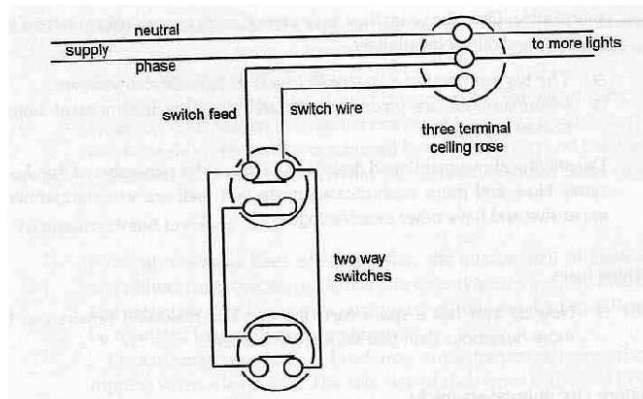

(9)

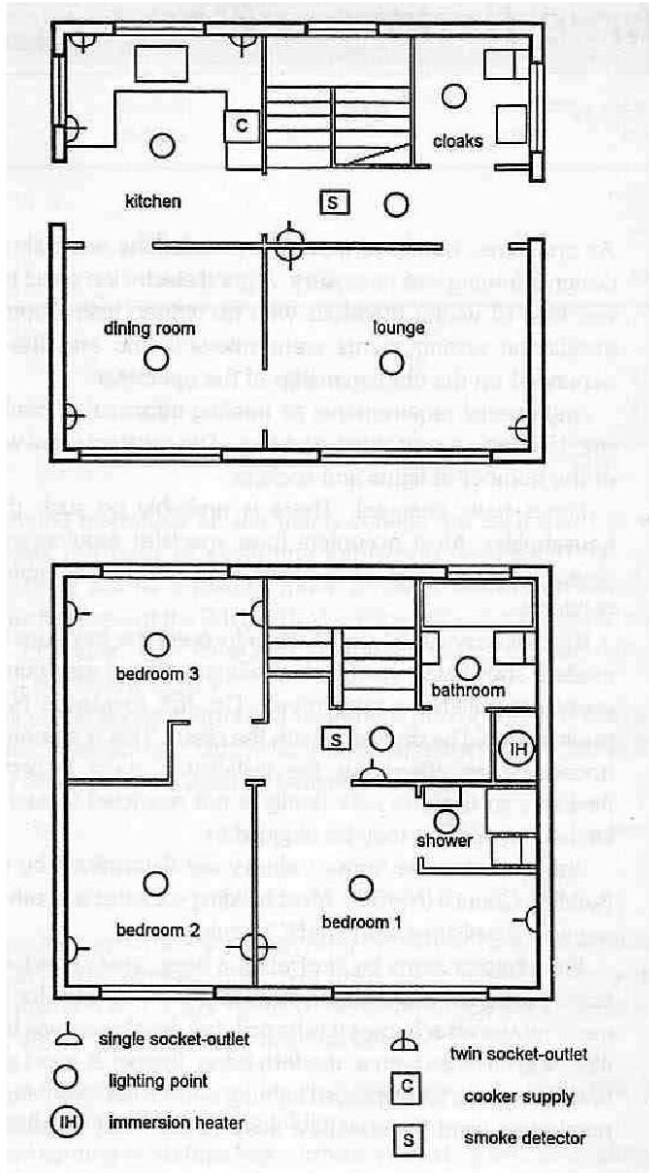

(10)

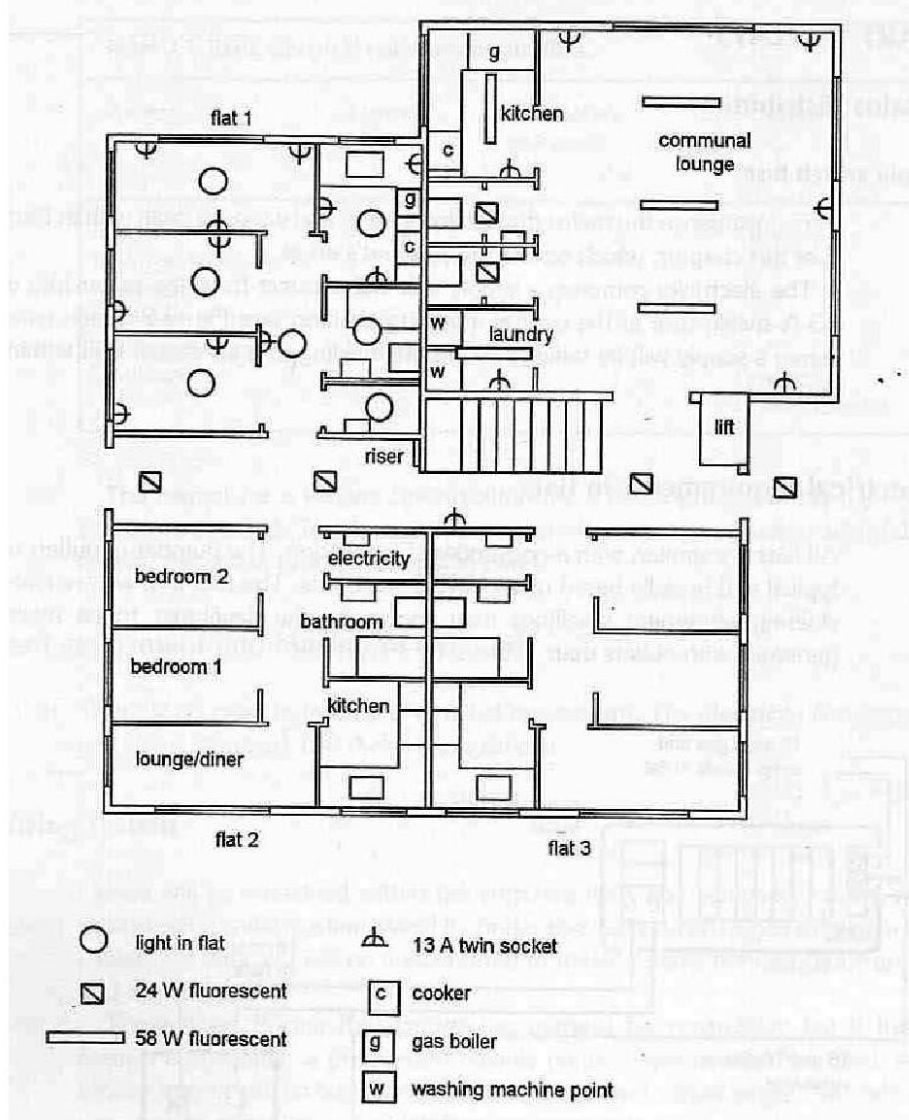

(11)

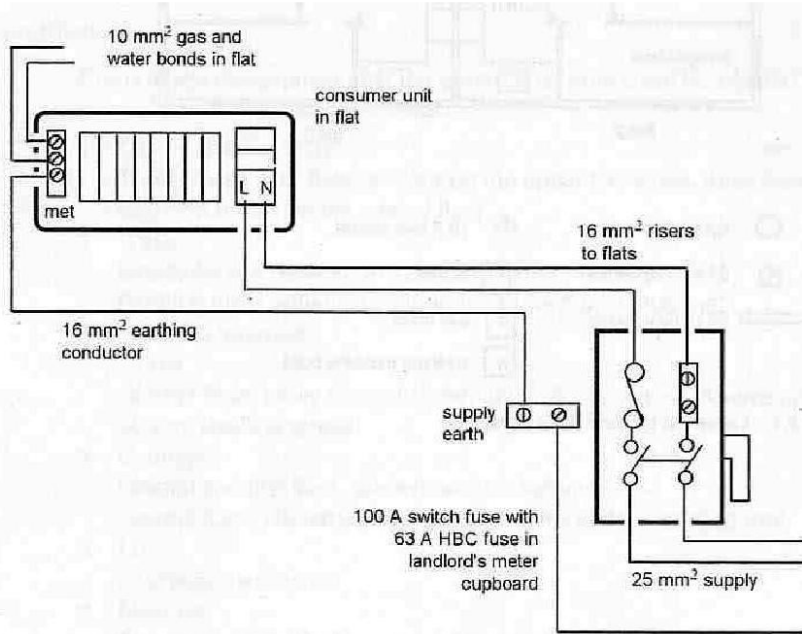


Figure 3.2 Distribution to flats.

(13)

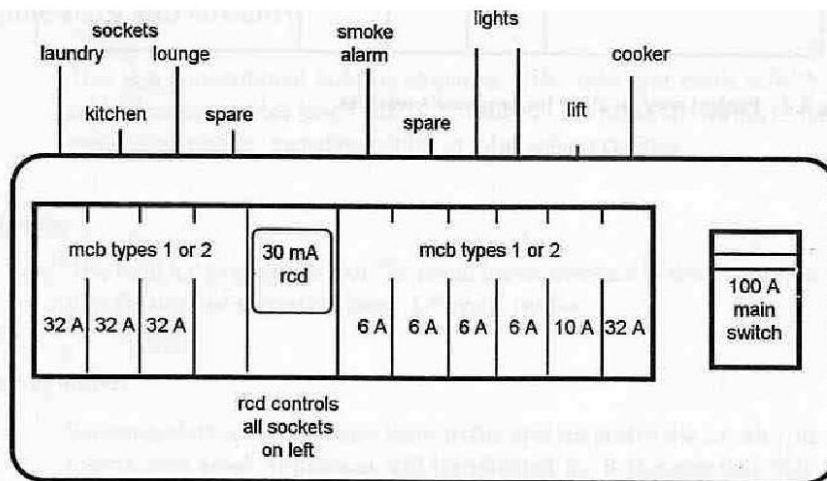


Figure 3.5 Landlord's distribution board.

## EE121 Electronics Power Control Devices

Study the followings

### TUTORING LESSONS


Lesson 1 Lesson 2

Then do the following exercises.

#### H026 Online Test

Ref473

Gain

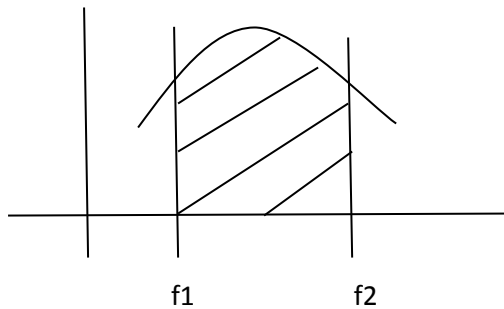

The given characteristics curve is

|        |                  |   |                  |
|--------|------------------|---|------------------|
| A      | High pass filter | B | Low pass filter  |
| C      | Band pass filter | D | Band stop filter |
| Answer |                  |   |                  |

Ref478

This equation is used for

1

$$f_c = \dots\dots\dots$$

$$6.28 \sqrt{R_1 R_2 C_1 C_2}$$

|   |  |   |   |
|---|--|---|---|
| A | First order high pass Butterworth filter | B | First order low pass Butterworth filter |
|---|--|---|---|




|               |  |   |   |
|---------------|--|---|---|
| C             | Second order low pass Butterworth filter | D | Second order high pass Butterworth filter |
| <b>Answer</b> |  |   |   |

Ref479

In 4 quadrant drive system, quadrant 4 is a function of

|               |                  |   |                 |
|---------------|------------------|---|-----------------|
| A             | Reversed braking | B | Forward driving |
| C             | Reversed driving | D | Forward braking |
| <b>Answer</b> |                  |   |                 |


Ref480

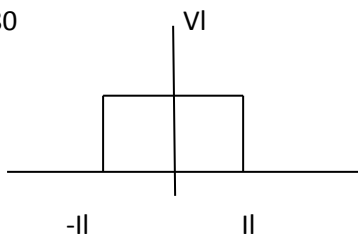

This characteristics stands for

|               |                 |   |                 |
|---------------|-----------------|---|-----------------|
| A             | Class A chopper | B | Class B chopper |
| C             | Class C chopper | D | Class D chopper |
| <b>Answer</b> |                 |   |                 |


Ref481

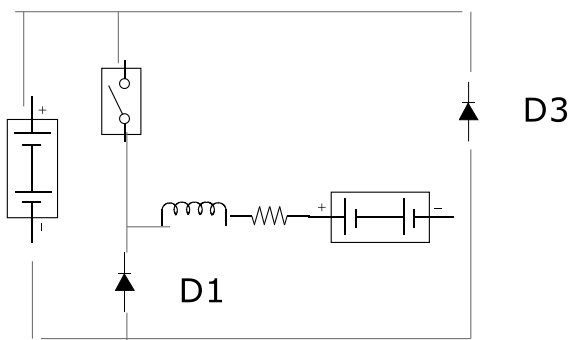

This is an equivalent circuit for


|        |                 |   |                 |
|--------|-----------------|---|-----------------|
| A      | Class A chopper | B | Class B chopper |
| C      | Class C chopper | D | Class D chopper |
| Answer |                 |   |                 |

Ref482

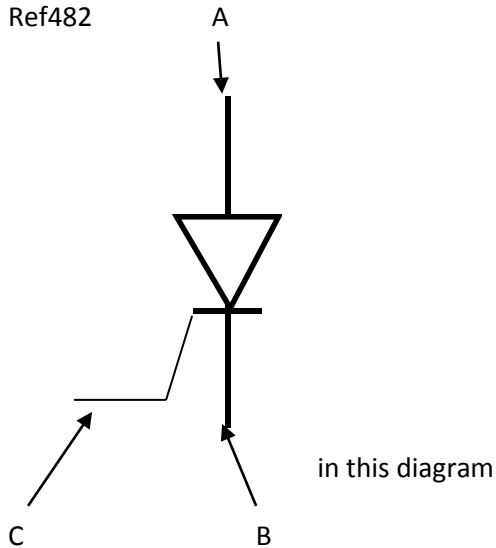

|        |                              |   |                              |
|--------|------------------------------|---|------------------------------|
| A      | A-Anode, B= Cathode, C- Gate | B | A-Gate, B= Cathode, C- Anode |
| C      | A-Cathode, B= Anode, C- Gate | D |                              |
| Answer |                              |   |                              |


Ref483

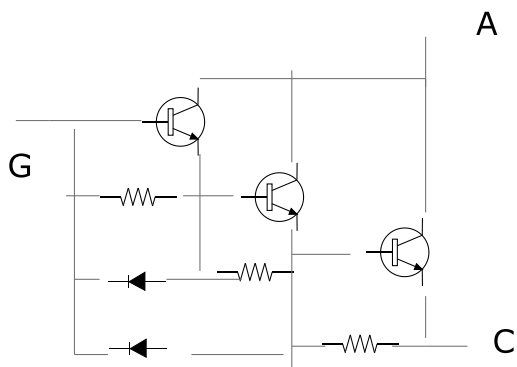

This circuit is

|        |   |   |                                      |
|--------|---|---|--------------------------------------|
| A      | Single stage Darlington pair transistor | B | Two stage Darlington pair transistor |
| C      | Three stage Darlington pair transistor  | D |                                      |
| Answer |   |   |                                      |

Ref484

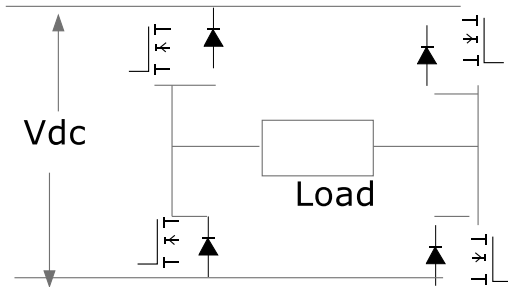

This circuit makes


|               |                 |   |                 |
|---------------|-----------------|---|-----------------|
| A             | DC-DC converter | B | AC-DC converter |
| C             | DC-AC Inverter  | D |                 |
| <b>Answer</b> |                 |   |                 |

Ref485

These converters are used to obtain a variable AC output voltage from a \_\_\_\_\_ and a single phase converter with a triac .

|               |                    |   |                 |
|---------------|--------------------|---|-----------------|
| A             | Variable dc source | B | Fixed dc source |
| C             | Variable ac source | D | Fixed ac source |
| <b>Answer</b> |                    |   |                 |

Ref486

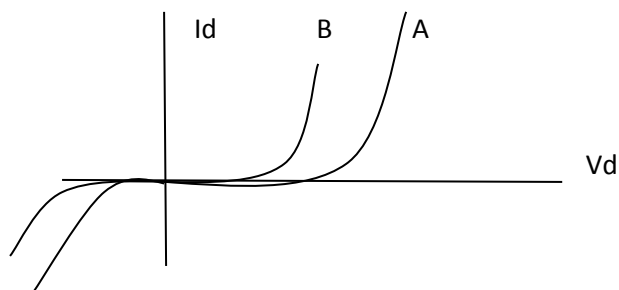

Curve A represents \_\_\_\_\_ & curve B represents \_\_\_\_\_.

|   |                                      |   |                                      |
|---|--------------------------------------|---|--------------------------------------|
| A | Hot carrier diode, PN Junction diode | B | PN Junction diode, Hot carrier diode |
| C |                                      |   |                                      |

|        |  |
|--------|--|
| Answer |  |
|--------|--|

Ref487

6 steps inverter can be used for

|        |                       |   |          |
|--------|-----------------------|---|----------|
| A      | Single phase AC motor | B | DC motor |
| C      | Three phase AC motor  |   |          |
| Answer |                       |   |          |

Ref488

RMS current produced by current source inverter is

|        |                                |   |                                 |
|--------|--------------------------------|---|---------------------------------|
| A      | $I_{1\text{ rms}} = 0.5 I_d$   | B | $I_{1\text{ rms}} = 0.78 I_d$   |
| C      | $I_{1\text{ rms}} = 0.707 I_d$ | D | $I_{1\text{ rms}} = 1.4142 I_d$ |
| Answer |                                |   |                                 |

## WK 12-EE206 AC Machines

### EE206 AC Machines

#### TUTORING LESSONS

[EE206 Part 1](#)   [EE206 Part 2](#)   [EE206 Part 3](#)

#### Test & Assessment

[http://www.filefactory.com/file/5stgiskbar09/n/G043\\_G045\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/5stgiskbar09/n/G043_G045_Online_Test_1_Answer_doc)

[http://www.filefactory.com/file/7h9o99zngfq1/n/G043\\_G045\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/7h9o99zngfq1/n/G043_G045_Online_Test_1_Question_pdf)

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

Study the EE206 file notes and do the exercises

G043+G045 Online Test

Ref374

Which is correct formula

|               |                                     |   |                                      |
|---------------|-------------------------------------|---|--------------------------------------|
| A             | $T = F \times r$<br>$P = 9.55 / NT$ | B | $T = F \times r$<br>$P = NT / 9.55$  |
| C             | $T = F + r$<br>$P = NT / 9.55$      | D | $T = F \times r$<br>$P = 9.55 / N+T$ |
| <b>Answer</b> |                                     |   |                                      |

Ref376

The heat taken away by blower is

|               |                         |   |                        |
|---------------|-------------------------|---|------------------------|
| A             | $P = 640V (t_2 - t_1)$  | B | $P = 320V (t_2 - t_1)$ |
| C             | $P = 1280V (t_2 - t_1)$ | D | $P = 160V (t_2 - t_1)$ |
| <b>Answer</b> |                         |   |                        |

Ref378

The 6 poles wound rotor induction motor is excited by three phase 60 HZ source. Calculate the rotor frequency for (a) Standstill (b) 500 rpm same direction (c) 500 rpm opposite direction.

|               |                     |   |                      |
|---------------|---------------------|---|----------------------|
| A             | 50HZ, 70 HZ, 170HZ  | B | 60HZ, 35 HZ, 85 HZ   |
| C             | 25 HZ, 35 HZ, 40 HZ | D | 15 HZ, 35 HZ, 125 HZ |
| <b>Answer</b> |                     |   |                      |

Ref380

A three phase induction motor having synchronous speed of 1200 rpm draws 80kw from three phase feeder. Copper loss & iron loss in stator amount to 5kw. If the motor runs at 11452 rpm, calculate the efficiency of motor.

|        |     |   |       |
|--------|-----|---|-------|
| A      | 45% | B | 87.5% |
| C      | 75% | D | 35%   |
| Answer |     |   |       |

Ref382

Locked rotor test is performed to determine.

|        |                |   |                   |
|--------|----------------|---|-------------------|
| A      | Core parameter | B | Winding parameter |
| C      | Load parameter | D | 35%               |
| Answer |                |   |                   |

Ref384

A three phase 208 V induction motor having synchronous speed 1200 rpm runs at 1140 rpm. When connected to 215V , driving at constant load, calculate the speed if voltage is 240V

|        |          |   |         |
|--------|----------|---|---------|
| A      | 1152 rpm | B | 800 rpm |
| C      | 700 rpm  | D | 500 rpm |
| Answer |          |   |         |

Ref386

The system that reverses the supply connection to the motor terminals when the stop switch is pressed is

|        |                 |   |                    |
|--------|-----------------|---|--------------------|
| A      | Dynamic braking | B | Plugging           |
| C      | Forward reverse | D | Time delay starter |
| Answer |                 |   |                    |

Ref388

A 500HP 720 rpm synchronous motor connected to 3980V three phase line generates an excitation voltage  $E_f=1790V$  (L-N) when the dc excitation current is 25 amp. The synchronous reactance is  $22\Omega$ , torque angle between  $E_f$  &  $V$  is  $30^\circ$ . Calculate shaft torque.

|        |          |   |          |
|--------|----------|---|----------|
| A      | 2000 N-m | B | 3715 N-m |
| C      | 1500 N-m | D | 750 N-m  |
| Answer |          |   |          |

Ref390

In a synchronous motor, when power factor is unity, the line current is

|        |           |   |         |
|--------|-----------|---|---------|
| A      | Maximum   | B | Minimum |
| C      | Unchanged | D |         |
| Answer |           |   |         |

Ref392

Under excitation makes the power factor of a synchronous machine to become

|        |         |   |         |
|--------|---------|---|---------|
| A      | Unity   | B | Leading |
| C      | Lagging | D |         |
| Answer |         |   |         |

### EE207 DC Machines

### EE207 DC Machines

### TUTORING LESSONS

[EE207 Part 1](#) [EE207 Part 2](#) [EE207 Part 3](#)

### Test & Assessment

[http://www.filefactory.com/file/2ejf6p7o0j0f/n/G044\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/2ejf6p7o0j0f/n/G044_Online_Test_1_Answer_doc)

Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

Password- [iqytechnicalcollege](#)

Study the EE207 File notes and do the exercises


**G044 Online Test**

Ref394

Power provided by dc generator is

|        |             |   |               |
|--------|-------------|---|---------------|
| A      | $P = B I V$ | B | $P = B L V I$ |
| C      | $P = B I L$ | D | $P = B L V$   |
| Answer |             |   |               |

Ref395

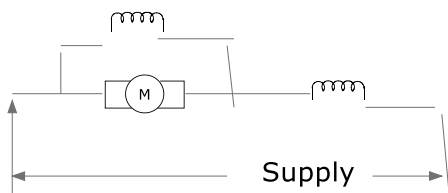

This connection is

|        |                      |   |                     |
|--------|----------------------|---|---------------------|
| A      | Series               | B | Shunt               |
| C      | Short shunt compound | D | Long shunt compound |
| Answer |                      |   |                     |

Ref396

Calculate the coil span for

- (a) 36 slots, 4 poles simplex lap (b) 36 slots, 2 poles, Duplex wave



|               |                            |   |                           |
|---------------|----------------------------|---|---------------------------|
| A             | 1 to 10, 1 to 39 & 1 to 35 | B | 1 to 9, 1 to 38 & 1 to 34 |
| C             | 1 to 8, 1 to 37 & 1 to 33  | D | 1 to 7, 1 to 36 & 1 to 32 |
| <b>Answer</b> |                            |   |                           |

Ref397

The brushes on a 0.4 m diameter commutator are rocked 0.03m circumferentially. The machine has 6 poles, simplex lap wound, 378 conductors 800 Armature current. Calculate cross magnetizing and de-magnetizing ampere turn / pole.

|               |                            |   |                             |
|---------------|----------------------------|---|-----------------------------|
| A             | 600 AT/pole, 1500 AT /pole | B | 1250 AT/pole, 3000 AT /pole |
| C             | 300 AT/pole, 750 AT /pole  | D | 150 AT/pole, 375 AT /pole   |
| <b>Answer</b> |                            |   |                             |

Ref398

Motor particulars 3.75 KW, 230V, 18A, 1750 rpm  $R_a=0.3\Omega$  , brush drop 2V on load.

Calculate final torque if field flux is reduced to 96%

|               |           |   |         |
|---------------|-----------|---|---------|
| A             | 50.56 N-m | B | 100 N-m |
| C             | 150 N-m   | D | 40 N-m  |
| <b>Answer</b> |           |   |         |

Ref399

7.5KW 230V 1750 rpm shunt motor, armature resistance  $0.35\Omega$ , shunt field resistance  $62.2\Omega$

If no load current is 7.7 amp, full load efficiency 86% , brush drop 3V at full load & 1 V at no load.

Calculate % regulation.

|               |      |   |     |
|---------------|------|---|-----|
| A             | 5.7% | B | 10% |
| C             | 12%  | D | 15% |
| <b>Answer</b> |      |   |     |

Ref400

The winding resistance of a 500V, 60KW dc shunt motor are  $R_a=0.2\Omega$   $R_f=200\Omega$ , mechanical losses are 1.4KW. Determine the efficiency of the machine.

(a) When the line current is 102.5A (b) At full load.

|        |          |   |               |
|--------|----------|---|---------------|
| A      | 70%, 75% | B | 90.93%, 90.9% |
| C      | 95%, 93% | D | 78%, 87%      |
| Answer |          |   |               |

Ref401

The resistance of an armature winding at 25°C was found to be 0.26Ω. After a heat run , it becomes 0.296Ω. Calculate the temperature rise of the winding.

|        |   |   |   |
|--------|---|---|---|
| A      | $\Delta t = 70\text{ }^{\circ}\text{C}$ | B | $\Delta t = 36\text{ }^{\circ}\text{C}$ |
| C      | $\Delta t = 15\text{ }^{\circ}\text{C}$ | D | $\Delta t = 12\text{ }^{\circ}\text{C}$ |
| Answer |   |   |   |

Ref402

A 75KW 500V generator has a voltage regulation 4% , calculate

- The open circuit voltage
- Assuming the voltage varies uniformly between no load and full load current. Calculate the KW output of a terminal voltage 510V.

|        |                |   |             |
|--------|----------------|---|-------------|
| A      | 500V, 20 KW    | B | 250V, 10 KW |
| C      | 520V, 38.25 KW | D | 500V, 10 KW |
| Answer |                |   |             |

Ref403

A 4 poles wound armature operating in a field of flux 0.01wb in wound with 360 armature conductors. Determine the expression of torque as a function of speed. If  $V_t=250\text{V}$  and  $R_a=0.1\Omega$ .

|        |              |   |              |
|--------|--------------|---|--------------|
| A      | 1000 – 1.3 N | B | 2000- 2N     |
| C      | 3000 – 4N    | D | 2860 – 1.38N |
| Answer |              |   |              |

Ref404

The resistance of the armature of a 240V dc shunt motor is 0.5Ω . It is required that the current at starting be limited to 200% of full load current & full load current is 15A.

Determine

- (a) Total resistance of armature current at starting
- (b) The number of studs on the starter
- (c)  $r_3$ .

|        |           |   |              |
|--------|-----------|---|--------------|
| A      | 8Ω, 4, 1Ω | B | 10Ω, 3, 0.5Ω |
| C      | 8Ω, 2, 1Ω | D | 4Ω, 2, 1Ω    |
| Answer |           |   |              |

Ref405

Which is not a dc motor braking method?

|        |                    |   |                 |
|--------|--------------------|---|-----------------|
| A      | Plugging           | B | Dynamic braking |
| C      | Mechanical braking | D | Ward Leonard    |
| Answer |                    |   |                 |

Ref 406

Which equipment does not produce ripple?

|        |               |   |                   |
|--------|---------------|---|-------------------|
| A      | PWM Switching | B | Rectifier circuit |
| C      | DC Generator  | D | PV Inverter       |
| Answer |               |   |                   |

EE202 Electrical Circuits ( Needs to do)

[EE202 Electrical Circuits](#)

[TUTORING LESSONS](#)

[EE202 Part 1](#) [EE202 Part 2](#) [EE202 Part 3](#)

[Test & Assessment](#)

[http://www.filefactory.com/file/52h82a0t0f3f/n/E025\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/52h82a0t0f3f/n/E025_Online_Test_1_Question_pdf)

[http://www.filefactory.com/file/1qw3qtpv9qd5/n/E025\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/1qw3qtpv9qd5/n/E025_Online_Test_1_Answer_doc)

[http://www.filefactory.com/file/4m4fl31kp6w3/n/G048\\_Online\\_Test\\_1\\_Answer\\_doc](http://www.filefactory.com/file/4m4fl31kp6w3/n/G048_Online_Test_1_Answer_doc)

[http://www.filefactory.com/file/713uwwk5vbel/n/G048\\_Online\\_Test\\_1\\_Question\\_pdf](http://www.filefactory.com/file/713uwwk5vbel/n/G048_Online_Test_1_Question_pdf)



SUBMIT THE SCANNED COPY OF ANSWER to



Dr Kyaw Naing

PO BOX 227

Marrickville, NSW 1475, Sydney, Australia

Password- [iqytechnicalcollege](#)

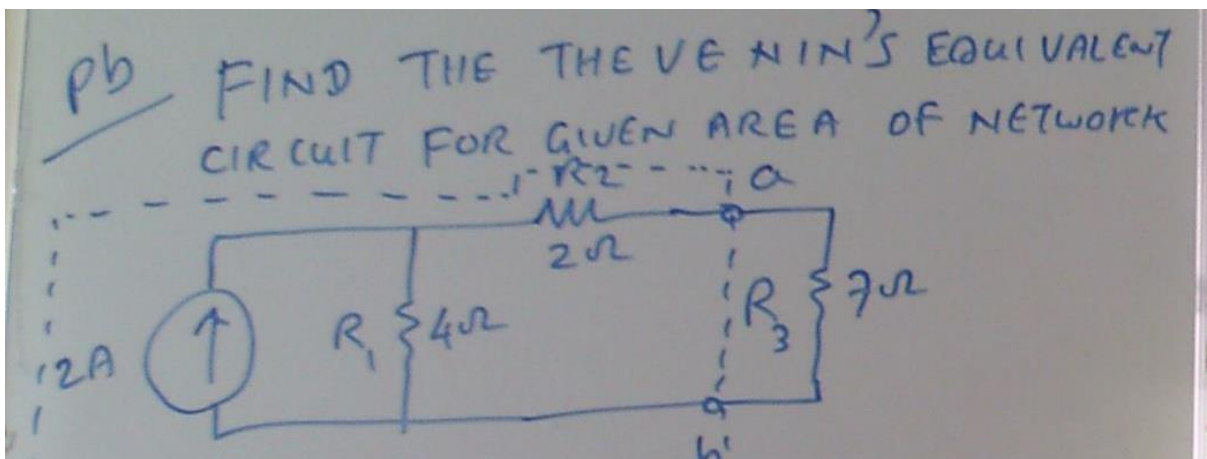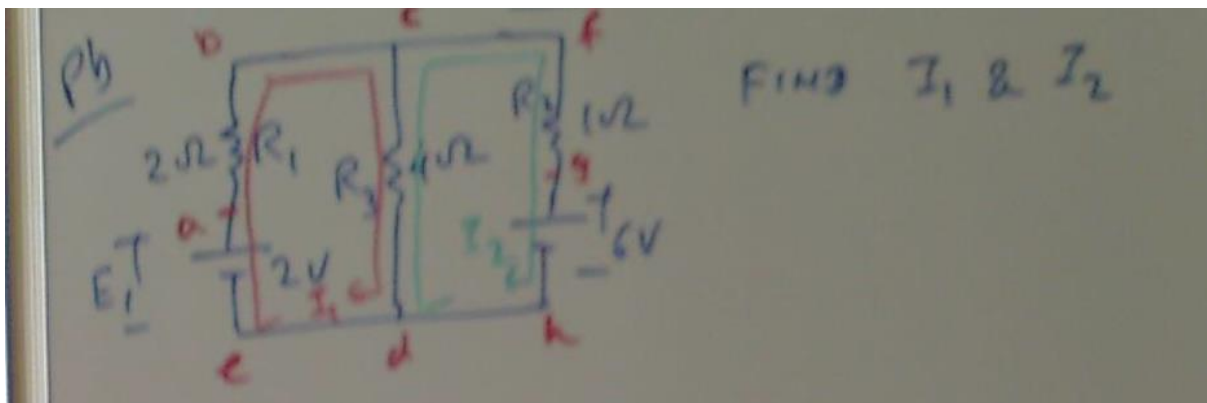

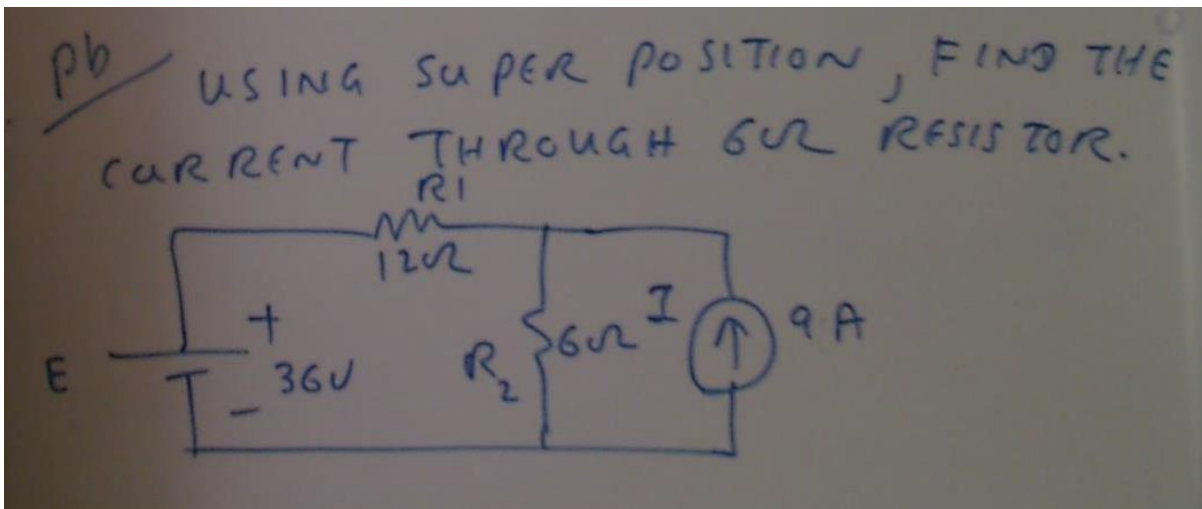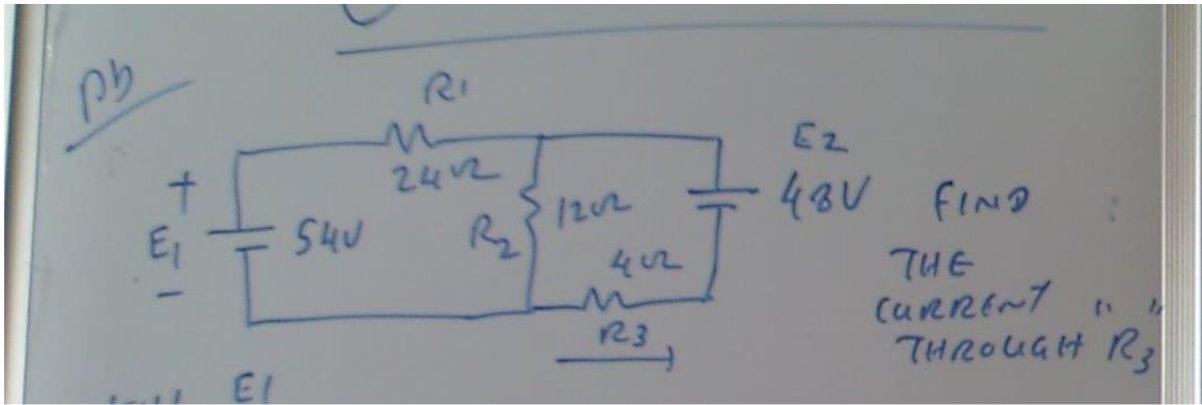

EE203 Three Phase Power Circuits ( Needs to do)

### EE203 Three Phase Power Circuits

### TUTORING LESSONS

[EE203 Part 1](#)   [EE203 Part 2](#)   [EE203 Part 3](#)

### Test & Assessment

[http://www.filefactory.com/file/49ibg1qt9fgh/n/G049\\_Online\\_Test\\_1\\_Answer.doc](http://www.filefactory.com/file/49ibg1qt9fgh/n/G049_Online_Test_1_Answer.doc)



[http://www.filefactory.com/file/5vhbs8sn20f3/n/G049\\_Online\\_Test\\_1\\_Question.pdf](http://www.filefactory.com/file/5vhbs8sn20f3/n/G049_Online_Test_1_Question.pdf)

SUBMIT THE SCANNED COPY OF ANSWER to

Dr Kyaw Naing

PO BOX 227

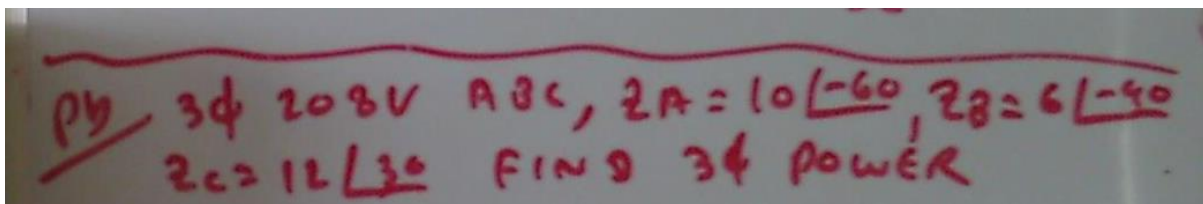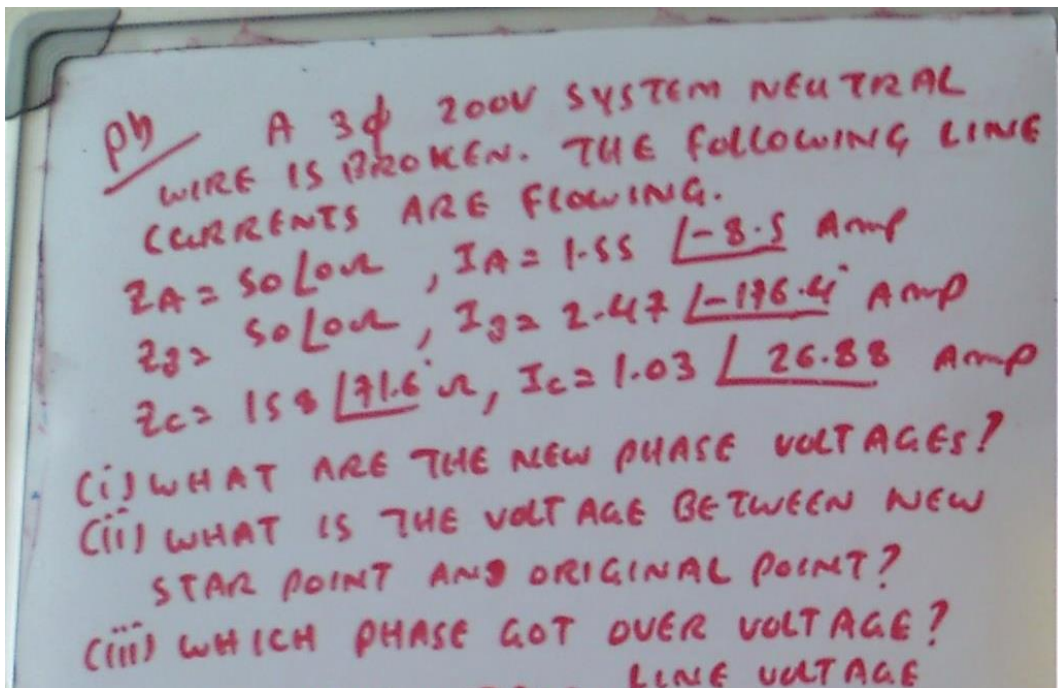Marrickville, NSW 1475, Sydney, Australia



ME 305 Corrosion Prevention ( Needs to do)

### TUTORING LESSONS

ME 305+ ME 209

#### Basic Theory/ Chemical effect on materials

Q1.

Explain chemical reaction inside electric cell.

Q2

Explain corrosion.

Q3

Describe the followings.

(a)Galvanic corrosion (b) Corrosion removal (c) Resistance

Q4

Write the ways to protect corrosion.

Q5

What are the forms of corrosion?

Q6

Express stress corrosion cracking.

Q7

Write notes for followings.

(a)Carbon steel (b)Stainless steel (c)Aluminium (d) Copper alloy

ME 306 Theory-of-waves-in-materials ( 1 pt) ( Needs to do)

## TUTORING LESSONS

ME306

Study ME 306 Folder & write the note on what you have read.

Slide 7

Q1.Explain elastic volume & shear wave

Slide 3

Q2.Explain basic wave phenomena

Slide 2

Q3.Write the equation for Clausius equality

ADDITIONAL REFERENCES

## MECHANICAL ENGINEERING LERCTURES

Certificate in Mechanical Trade Study Guide

BE (CIVIL & MECHANICAL) ENGINEERING INTERNATIONAL COURSE OUTLINE

Bachelor of Engineering (Mechanical) Year 3 ,4 & 5 Course Contents

[Bachelor of Engineering \(Civil\) Year 3 ,4 & 5 Course Contents](#)

## **CERTIFICATE (ELECTRICAL/CIVIL/MECHANICAL) INTERNATIONAL COURSE OUTLINE**

[Certificate in Electrical Engineering \(Certificate III in Electro-technology-Electrician\)](#)

[Certificate III in Electro-technology-Electrician](#)

[Certificate in Civil Engineering \(Certificate in Construction Studies\)](#)

[Certificate in Mechanical Engineering](#)

[Professional Certificate in Air-conditioning and Refrigeration \(BAE511+ME511\)](#)

### **Mechanical Engineering**

[Certificate+ Diploma+ Advanced Diploma of Mechanical Engineering Course Outline](#)

[Certificate in Mechanical Engineering \(CD Based Learning Instructions\)](#)

[Diploma of Mechanical Engineering \(CD Based Learning Instructions\)](#)

[Advanced Diploma of Mechanical Engineering \(CD Based Learning Instructions\) Part 1](#)

[Advanced Diploma of Mechanical Engineering \(CD Based Learning Instructions\) Part 2](#)

[Bachelor of Engineering \(Mechatronics\) +Advanced Diploma of Mechanical Engineering  
Course outline](#)

[Professional Certificate in Engineering Metallurgy \(BAE612\)](#)

[BAE 612 Part 1](#)

[BAE 612 Part 2](#)

[K131 + EE 308](#)







